



TCET/FRM/IP-02/12

**Term Work Index Sheet**  
 (To be filled up on regular basis)

Revision: A

Sr. No.	Name	DOP	DOC	Marks Obtain ed (100)	Signature of Faculty
<b>Basic Experiments</b>					
1	Mesh and Nodal Analysis	18-2	25-2	92	
2	Superposition Theorem	25-2	4-3	87	
3	Thevenin's and Maximum Transfer Theorem	4-3	9-3	85	
4	Series Resonance	9-3	16-3	93	
5	Circuits for SC and OC Test	16-3	18-3	95	
6	Slip Ring Induction Motor	18-3	25-3	96	
7					
8					
<b>Design Experiments / Project / Case Study</b>					
9					
10					
11					
12					
13					
14					
<b>Formative Assessment / Seminar / Remedial work / Assignments</b>					
15	7 Tutorials	18-2	25-3	93	
16					
17					
18					

DOP – Date of Performance. DOC – Date of Completion

**Certificate**

This is to Certify that Ms. **ISHIKA NEERAJ SHARMA** Class **AI&DS** Roll no. **45** Course **B.Tech** has successfully completed the term work requirements in the Subject **Basic Electrical Engineering** during the academic Year **2020-2021**.

Signature of faculty

Date:

Signature of HOD

Date:

Signature of Dean  
(Academic)

Date:

### LAB EVALUATION SHEET

Cycle-1  
Experiment/Tutorial No.: 1-3

Roll No.: 45

Parameters	Weightage	Category	Performance					
			Excel-lent (5)	Very Good (4)	Good (3)	Average (2)	Below Average (1)	Score
Technical Knowledge (Preparedness and Execution)	30	Prerequisites (2)	✓					
		Skills in performing experiment (2)						
		Learning (1)						
Technical Documentation (Developing skills for Journal Writing and Maintenance of Lab Notebook)	30	Format (1)		✓				
		Contents as per Format (2)						
		Quality (2)						
Level of Interaction (Developing Expression Power)	10	Level of Understanding (2)		✓				
		Questions & Answers (2)						
		Application (1)						
Behavioral (Attitude Towards Learning)	10	Attitude (1)	✓					
		Regularity (2)						
		Team Work / Group Activity(2)						
Compliance (Attainment of Objectives / Outcomes)	20	Course Objective Attainment (3)	✓					
		Learning Objective Attainment (2)						
<b>Total</b>	<b>100</b>							

Signature of Subject Teacher

### LAB EVALUATION SHEET

Cycle-2  
Experiment/Tutorial No.: 4-6

Roll No.: 45

Parameters	Weightage	Category	Performance					
			Excel-lent (5)	Very Good (4)	Good (3)	Average (2)	Below Average (1)	Score
Technical Knowledge (TK) (Preparedness and Execution)	30	Prerequisites (2)	✓					
		Skills in performing experiment (2)						
		Learning (1)						
Technical Documentation (TD) (Developing skills for Journal Writing and Maintenance of Lab Notebook)	30	Format (1)		✓				
		Contents as per Format (2)						
		Quality (2)						
Level of Interaction (LI) (Developing Expression Power)	10	Level of Understanding (2)	✓					
		Questions & Answers (2)						
		Application (1)						
Behavioral (B) (Attitude Towards Learning)	10	Attitude (1)	✓					
		Regularity (2)						
		Team Work / Group Activity(2)						
Compliance (C) (Attainment of Objectives / Outcomes)	20	Course Objective Attainment (3)	✓					
		Learning Objective Attainment (2)						
<b>Total</b>	<b>100</b>							

Signature of Subject Teacher

### Evaluation Index Sheet

Sr. No	Cycle	Expt. No.	TK	TD	LI	B	C	Total
1	Cycle-1	1-3	30	24	8	10	20	92
2	Cycle-2	4-6	30	24	10	10	20	94
		Total	60	48	18	20	20	186
		Average	30	24	9	10	20	93

Signature of Subject Teacher



Zagdu Singh Charitable Trust's (Regd.)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified \* Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

Ishika Sharma  
FE - A14 D5  
4B

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 1


Page :- 1

Date :- 18/2/2021


## EXPERIMENT NO. 1

### MESH AND NODAL ANALYSIS

## Electrical Circuit Diagram

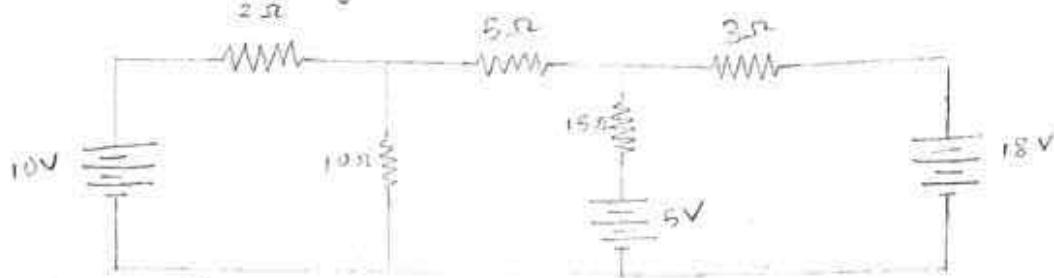

## Practical Circuit Diagram

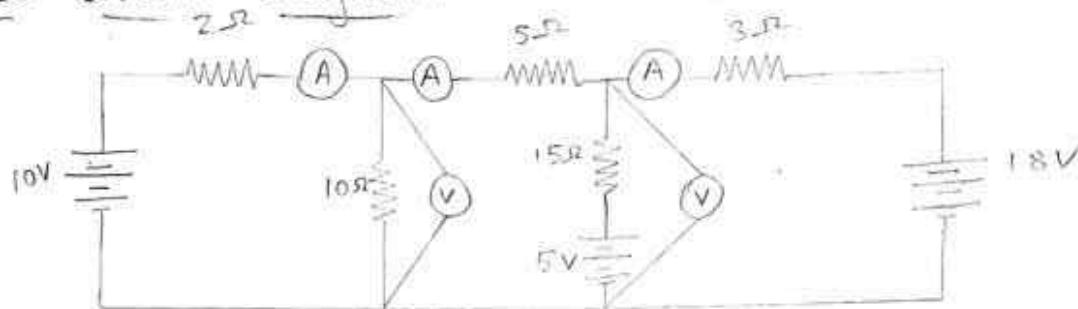

## Noval Analysis:

$v_1$		$v_2$	
calculated	observed	calculated	observed
9.69 V	9.70 V	13.78 V	13.8 V

Calculations: Applying KCL to  $v_A$ ,

$$I_1 + I_2 + I_3 = 0$$

$$\frac{v_A - 10}{2} + \frac{v_A - v_B}{5} + \frac{v_A - 0}{10} = 0$$

$$\therefore 8v_A - 2v_B = 50 \quad \text{--- (1)}$$

Applying KCL to  $v_B$ ,

$$I_4 + I_5 + I_6 = 0$$

$$\frac{v_B - v_A}{5} + \frac{v_B - 5}{15} + \frac{v_B - 18}{3} = 0$$

$$\therefore 9v_B - 3v_A = 95 \quad \text{--- (2)}$$

$\therefore$  On solving eqn 1 & 2

$$v_A = \underline{\underline{9.69}} \text{ V} \quad , \quad v_B = \underline{\underline{13.78}} \text{ V}$$



Zigdu Singh Charitable Trust's (Regd.)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC) Bangalore

Ishika Sharma

FE - A1 E&DS

45

Subject :- BEF

Experiment / Tutorial / Assignment No. :- |


Page :- 2

Date :- 18/12/2021


AIM : To perform Mesh and Nodal Analysis for the given circuits.

APPARATUS : Digital multimeter, power supply, resistors, bread board, wires

## Electrical Circuit Diagram:

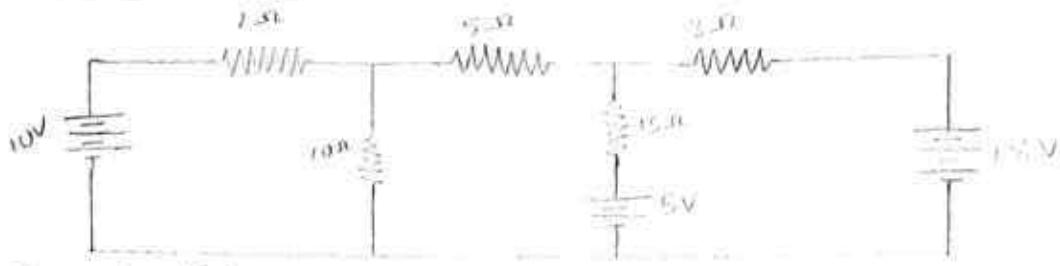

## Practical Circuit Diagram:

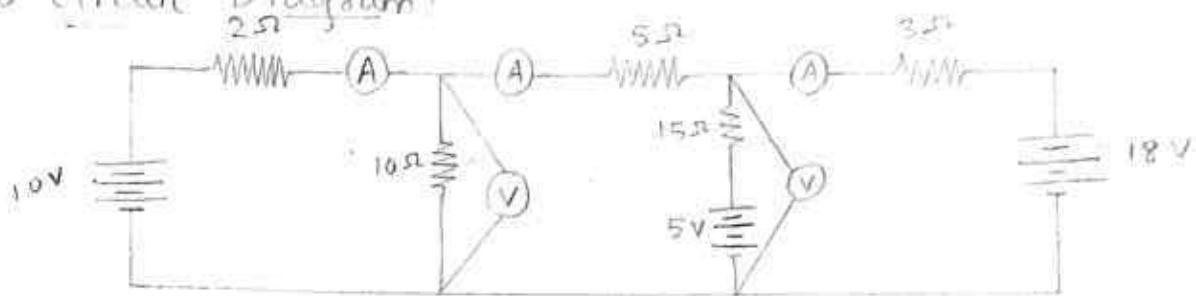

## Mesh Analysis:

$I_1$		$I_2$		$I_3$	
Calculated	Observed	Calculated	Observed	Calculated	Observed
0.151 A	152 mA	-0.818 A	-818 mA	-1.404 A	-1.40 A

Calculations : In Mesh 1, Applying KVL,

$$-2I_1 - 10(I_1 - I_2) + 10 = 0 \\ -12I_1 + 10I_2 = -10 \quad \text{--- (1)}$$

Applying KVL in mesh 2,


$$-5I_2 - 15(I_2 - I_3) - 5 - 10(I_2 - I_1) = 0 \\ 10I_1 - 30I_2 + 15I_3 = 5 \quad \text{--- (2)}$$

Applying KVL in mesh 3,

$$-3I_3 - 18 + 5 - 15(I_3 - I_2) = 0 \\ 15I_2 - 18I_3 = 13 \quad \text{--- (3)}$$

∴ On solving eq<sup>n</sup> 1, 2 & 3
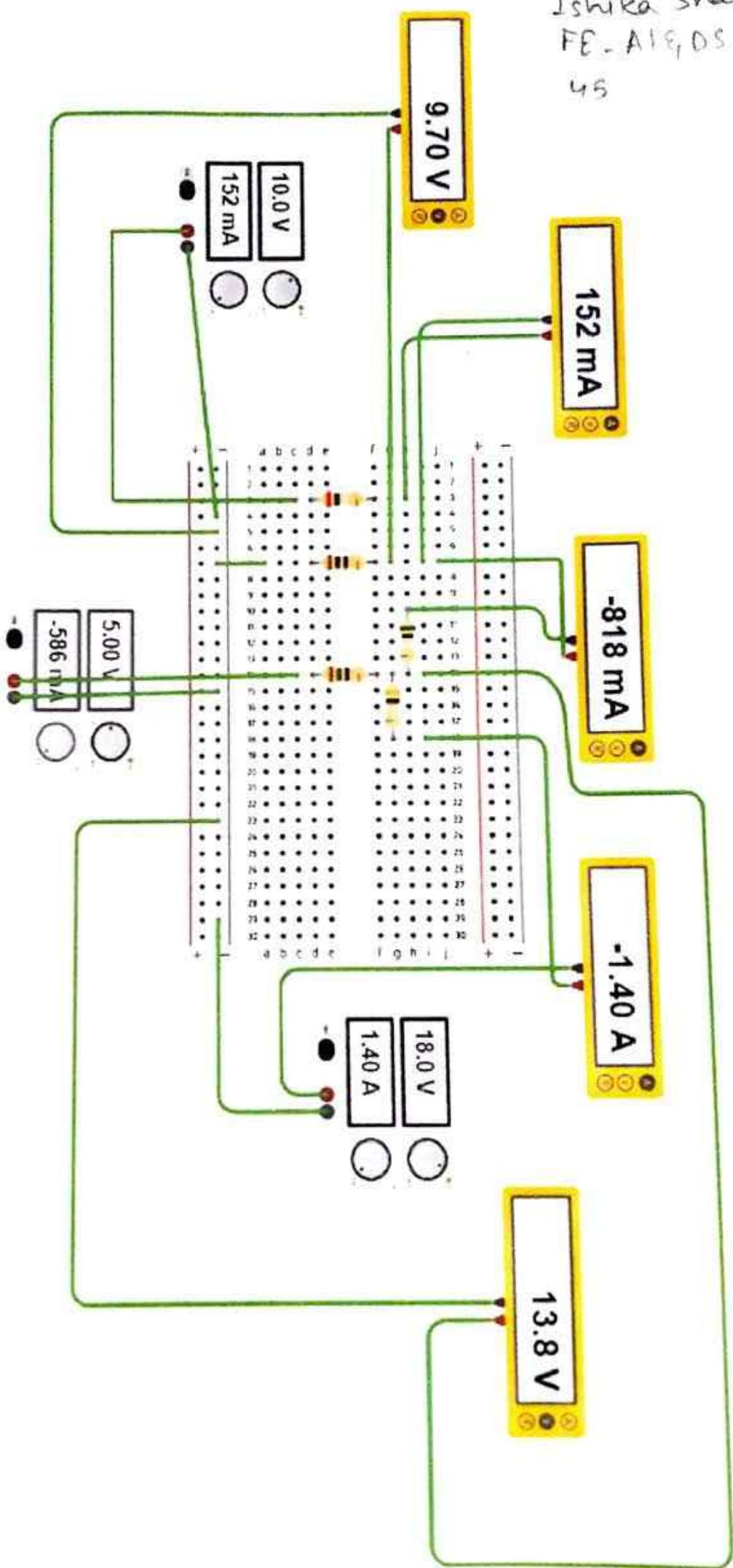
$$I_1 = 0.151 \text{ A}, \quad I_2 = -0.818 \text{ A}, \quad I_3 = -1.404 \text{ A}$$



**THAKUR COLLEGE OF  
ENGINEERING & TECHNOLOGY**

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 19<sup>th</sup> in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma  
FE-A1E DS

45

Subject :- B E E

Experiment / Tutorial / Assignment No. :- |

Page :- 3

Date :- 18/2/2021

CONCLUSION : Hence by applying Mesh and Nodal analysis current and voltage across any resistance can be calculated.

QUIZ :

1]

what is the use of breadboard and multimeter?

The purpose of breadboard is to make quick electrical connections between components like - resistors, LEDs, etc. Multimeter is a device used to measure voltage, current &amp; resistance.

2)

what do you require mesh &amp; nodal analysis?

In analysing a circuit using KCL, one can either do nodal analysis or Mesh analysis using KVL.

3)

Define voltage &amp; current.

Voltage is the difference in charge between 2 points. Current is the rate at which charge is flowing.

Objective	PRO 1	PRO 2	PRO 3	TOTAL	ES&H DEPARTMENT TCET
Weight	20	30	30	Score	Date of Performance : 18/2/21
Points					Date of Correction :
Score					Roll No : 45
Earned Points (EP) = Total Score / Marks in 100 =	100	Marks in 100 = EP * 20		Marks : _____ / 100	signature of Faculty : _____



Zagdu Singh Charitable Trust's (Regd.)

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma

FE - A18 DS

45

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 2


Page :- 1

Date :- 25/12/2021

## EXPERIMENT NO. 2

### VERIFICATION OF SUPERPOSITION

#### THEOREM

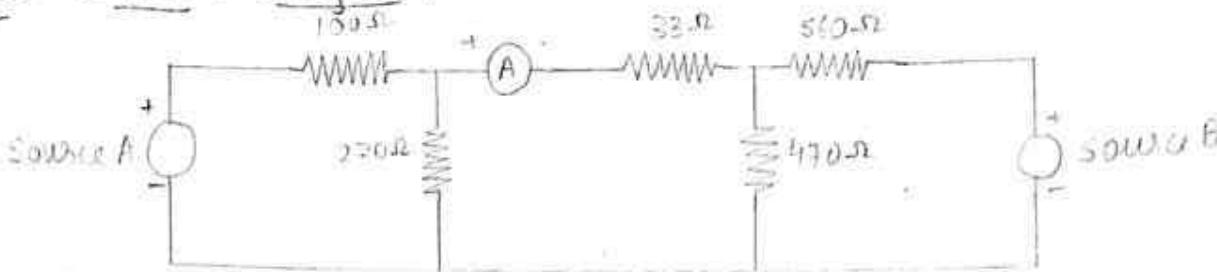Electrical Circuit Diagram:

SOURCE A : 12V  
 SOURCE B : 5V  
 Resistor under observation :  $33\Omega$

Observation Table:

	PRO 2				PRO 3	
	A = 12V	I <sub>A</sub> (mA)		I <sub>B</sub> (mA)	I <sub>Actual</sub> (mA)	
		Cal.	Obs.	Cal.		
	12V	23.8	23.1	6.4	6.39	16.6
	5V					16.7

Calculations: At Node 1,

$$\frac{V_1}{100} + \frac{V_1}{220} + \frac{V_1 - V_2}{33} = 0 \quad \text{--- (1)}$$

Now  $V_1 +$

At Node 2,

$$\frac{V_2}{470} + \frac{V_2 - 5}{560} + \frac{V_2 - V_1}{33} = 0 \quad \text{--- (2)}$$

$$I'_{33\Omega} = \frac{V_1 - V_2}{33}$$

$$I''_{33\Omega} = \frac{V_2 - V_1}{33}$$

$$I'_{33\Omega} = 0.023 \text{ A } (\rightarrow)$$




$$I''_{33\Omega} = -0.0064 \text{ A } (\leftarrow)$$

$$I_{33\Omega} = I'_{33\Omega} + I''_{33\Omega}$$

$$= 0.023 + (-0.0064)$$

$$= 0.023 - 0.0064$$
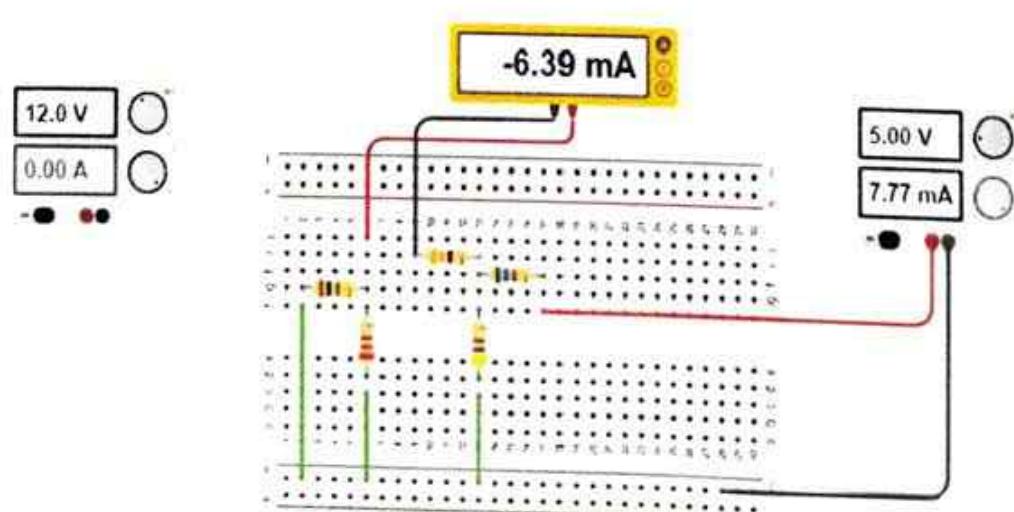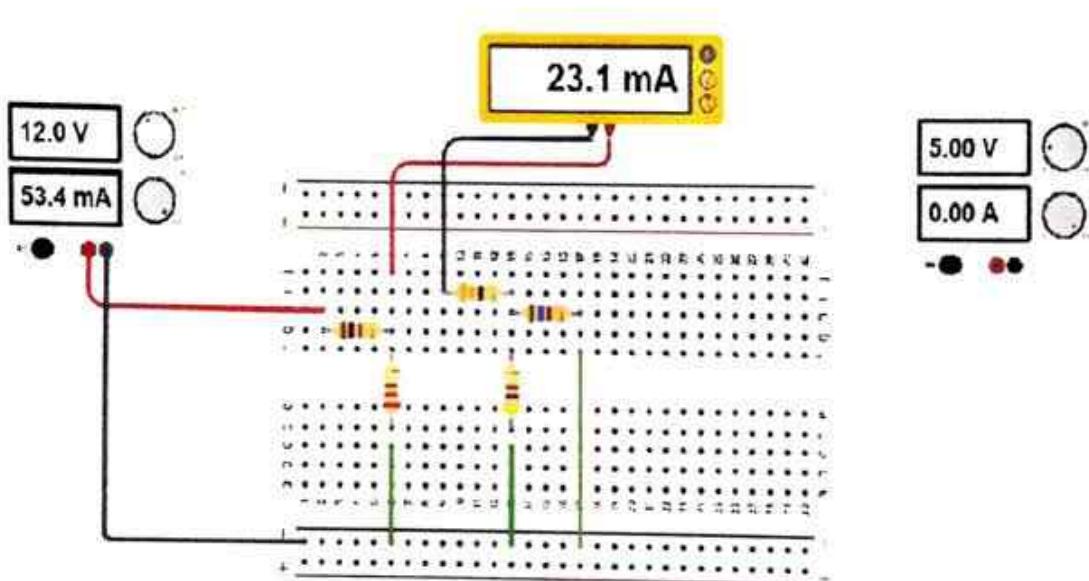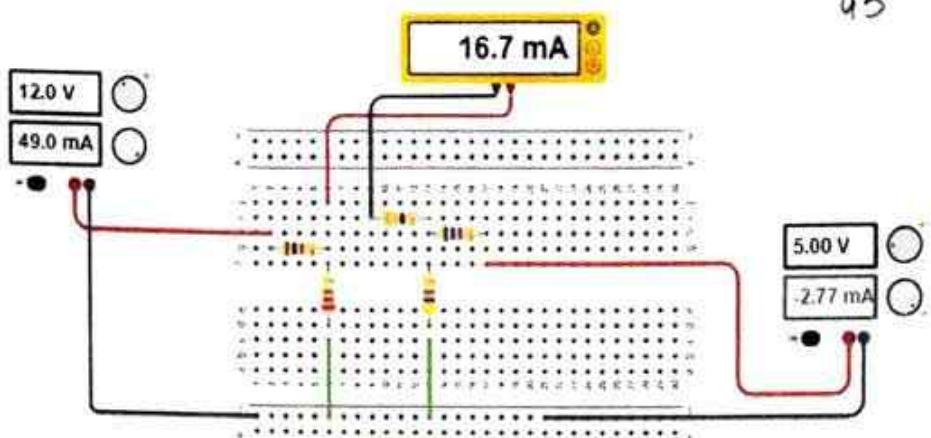
$$I_{33\Omega} = 0.0166 \text{ A } (\rightarrow)$$





Lagdu Singh / Date : 25/12/2021

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country. Ranked 195<sup>th</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified \* Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma  
FE-A1E, DS  
45

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 2

Page :- 2

Date :- 25/12/2021

AIM : To verify Superposition Theorem

APPARATUS : Digital Multimeter, Power supply, Resistor, Bread board, and connecting wires.

**THAKUR COLLEGE OF  
ENGINEERING & TECHNOLOGY**

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma  
FE\_A18\_D5  
45

Estd. in 2001

Subject :- BEF

Experiment / Tutorial / Assignment No. :- 2

Page :- 3

Date :- 25/2/2021

CONCLUSION: In any bilateral network having more than one source current in any resistance can be found out by algebraic sum of currents that would flow when each source is acting independently and other is replaced by its internal resistance. This was verified through our experiment wherein we took 12V and 5V individually and calculated the current through  $33\Omega$ . On algebraically adding the two currents, we get the value of the current when both 12V and 5V are acting together. This verifies the superposition theorem.

PRECAUTIONS: A learner has to:

- 1] Mount & unmount the resistors carefully.
- 2] Be careful while checking the values of voltages before switching on the circuit.

Objective	PRO1	PRO2	PRO3	Total Score	ES&H DEPARTMENT- TCET
weight	20	30	30		Date of Performance : 25/2/21
Points					Date of Correction:
Score					Roll NO: 45
Earned Points (EP) = Total Score			60	Marks : _____ /100	Signature of Faculty:

**THAKUR COLLEGE  
OF  
ENGINEERING & TECHNOLOGY**

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 195 in NIRF India Ranking 2019 in Engineering College category

• ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA) New Delhi

• Institute Accredited by National Assessment and Accreditation Council (NAAC) Bangalore

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 3

Page :- 1

Date :- 4/3/2021




Ishika Sharma  
FE - A1E05  
45

# EXPERIMENT NO. 3


## MAXIMUM POWER TRANSFER &

## THEVENIN'S THEOREM

## Circuit Diagram

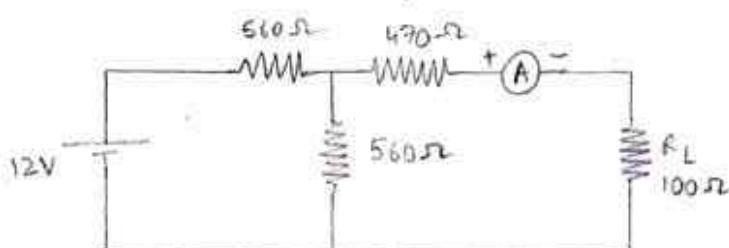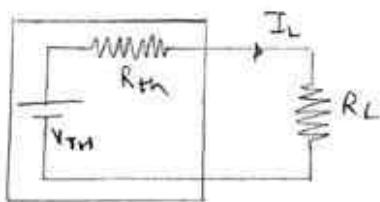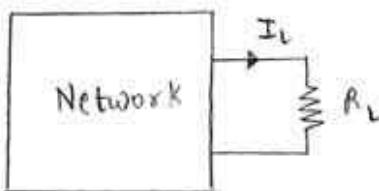

Any Complex Network

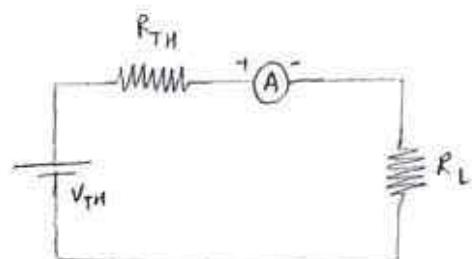

Thevenin's Equivalent Circuit

## OBSERVATION :

Thevenin's Theorem : PRO 1

	observed	calculated
$V_{TH}$ (V)	6V	6V
$R_{TH}$ ( $\Omega$ )	750 $\Omega$	750 $\Omega$
$I_L$ (mA)	7.06mA	7.06mA

## CALCULATION :

Cal calculating  $V_{TH}$ :

Applying KVL in mesh 1,

$$-560I_1 - 560(I_1 - I_2) + 12 = 0$$

$$-560I_1 - 560I_1 + 560I_2 = -12$$

$$-1120I_1 + 560I_2 = -12 \quad \text{---(1)}$$

$$\therefore -1120I_1 = -12$$

( $\because I_2 = 0A$ )

$$I_1 = 0.0107A$$

Applying KVL in mesh 2,

$$-470 - V_{TH} - 560(I_2 - I_1) = 0$$

$$-470 + 560I_1 = V_{TH}$$

$$-470 + 560(0.0107) = V_{TH}$$

$$V_{TH} = 6V$$

AIM : To verify Maximum Power transfer & Thevenin's theorem

APPARATUS : Digital Multimeter, Power supply, Resistors, Bread Board and connecting wires.

RESULT AND DISCUSSION : PRO 1: Verification of values theoretically and practically verifies Thevenin's Theorem.

PRO 2: Verification of values theoretically and practically verifies Maximum Power Transfer Theorem.

CONCLUSION : Hence when load resistance is equal to internal resistance of the network ( $R_{TH}$ ) maximum power is transferred to the load. This was verified by taking a constant value of  $R_{TH}$  and five different values of  $R_L$ . When  $R_{TH} = R_L$ , the value of power dissipated across  $R_L$  is maximum and decreases otherwise. This verifies maximum power transfer theorem.


### QUIZ :

1] State Thevenin's Theorem.

→ "Any two terminals of a network can be replaced by an equivalent voltage source and an equivalent series resistance."

calculating  $R_{TH}$

$$R_{TH} = 750\Omega$$

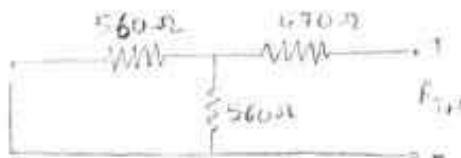

calculating  $I_L$ ,  $R_L = 100\Omega$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{6}{750 + 100} = 7.06 \text{ mA}$$



$$I_L = 7.06 \text{ mA}$$

### PRO 2: OBSERVATION:

$R_{TH}$	$R_L$	$I_L$ (calc)	$I_L$ (obs.)	$P_{RL}(\text{mW})$	$I^2 R_L$
				Calcult.	Observ.
750Ω	100Ω	7.06mA	7.06mA	4984	4984.3
750Ω	470Ω	4.9mA	5mA	11284	11150
750Ω	750Ω	4mA	4mA	12000	12000
750Ω	1kΩ	3.4mA	3.42mA	11560	11696.6
750Ω	1.47kΩ	2.7mA	2.7mA	10716.5	10716.5

### CALCULATIONS:

$$1) I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{6}{750 + 100} = 7.06 \text{ mA}$$

$$P_{RL} = I^2 R_L = (7.06)^2 \times 100 = 4984 \text{ mW}$$

$$2) I_L = \frac{6}{750 + 470} = 4.9 \text{ mA}$$

$$P_{RL} = (4.9)^2 \times 470 = 11284 \text{ mW}$$

$$3) I_L = \frac{6}{750 + 750} = 4 \text{ mA}$$

$$P_{RL} = (4)^2 \times 750 = 12000 \text{ mW}$$



$$4) I_L = \frac{6}{750 + 1000} = 3.4 \text{ mA}$$

$$P_{RL} = (3.4)^2 \times 1000 = 11560 \text{ mW}$$

$$5) I_L = \frac{6}{750 + 1470} = 2.7 \text{ mA}$$

$$P_{RL} = (2.7)^2 \times 1470 = 10716.5 \text{ mW}$$

Ishika Sharma  
FE-AI&DS  
45

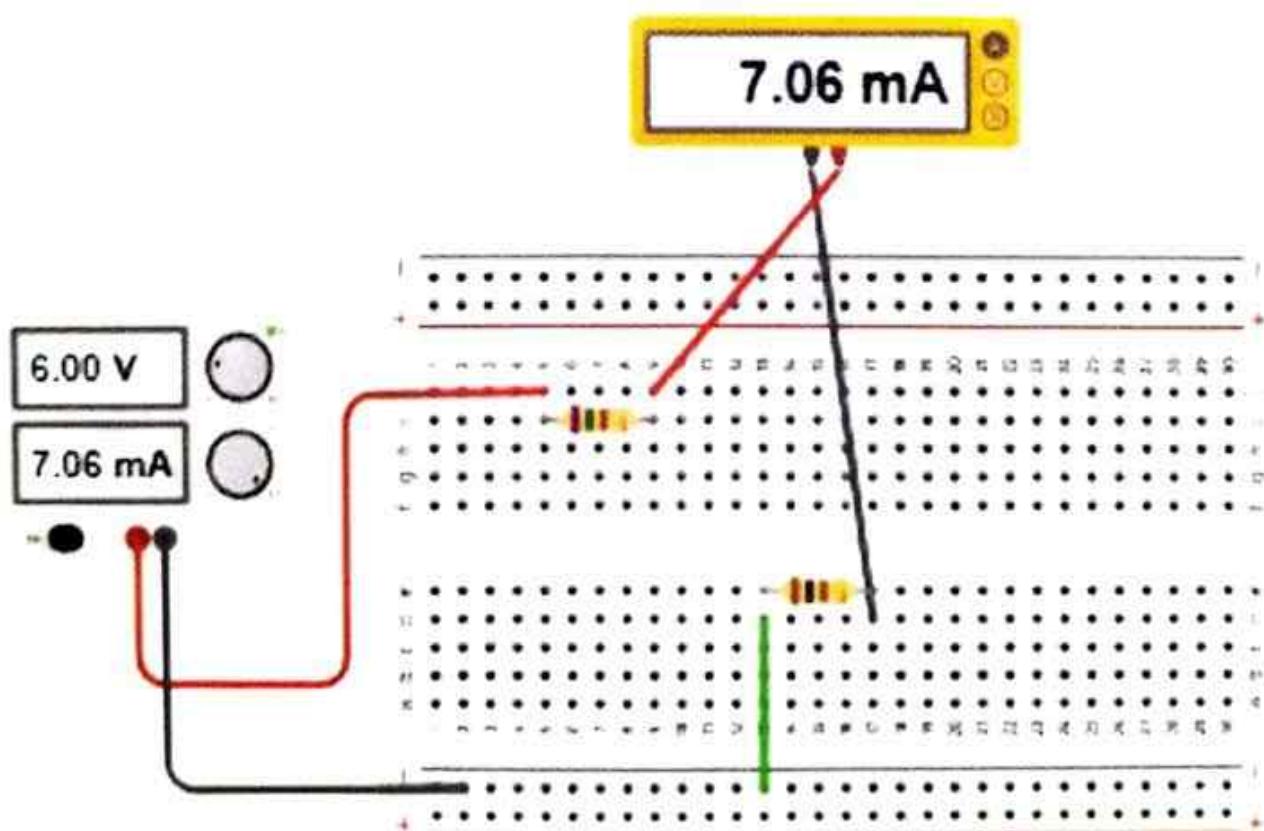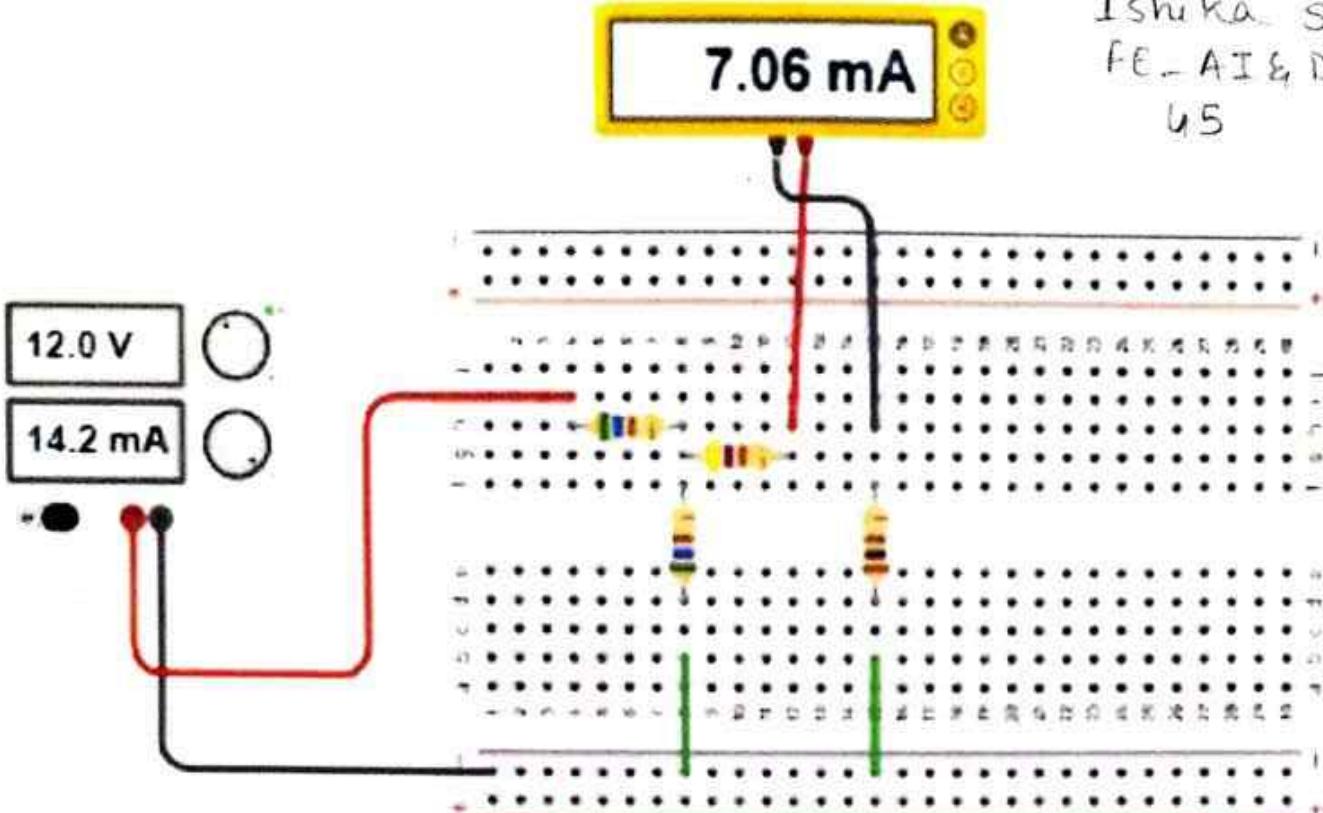

Q] →

State Maximum Power Transfer Theorem.

"The maximum power is delivered from a source to a load when the load resistance is equal to the source resistance."

Objective	PRO 1	PRO 2	PRO 3	Total	H & S DEPARTMENT - TCET
Weight	20	30	30	Score	Date of Performance: 4/3/21
Points					Date of Correction:
Score					Roll No: 45
Earned Points (EP) = Total Score/100 Marks in 100 = Marks : / 100				EP * 20	Signature of Faculty:
=					



Zagdu Singh Charitable Trust's (Regd.)

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 195<sup>th</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma  
FE-AI&DS

45

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 4



Page :- 1

Date :- 9/3/2021

EXPERIMENT NO. 4

SERIES      RESONANCE

### CIRCUIT DIAGRAM:

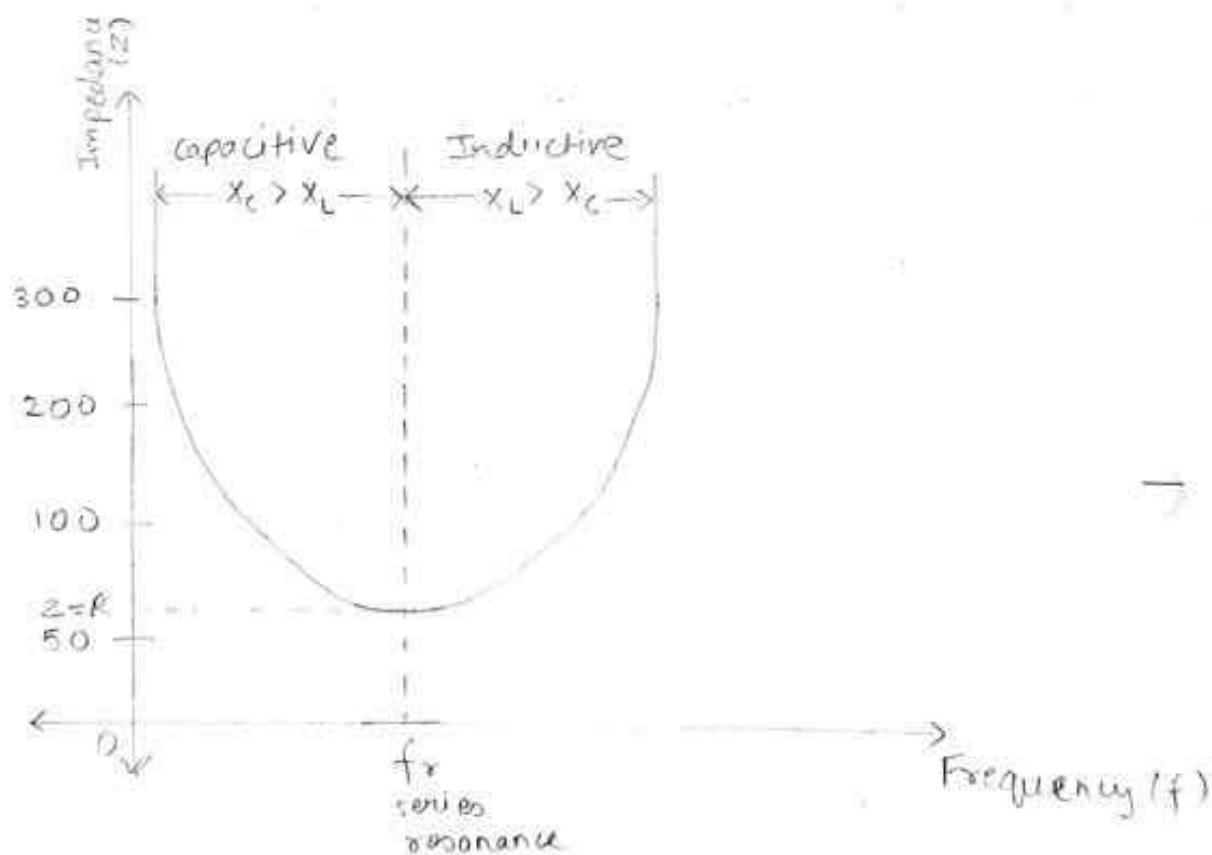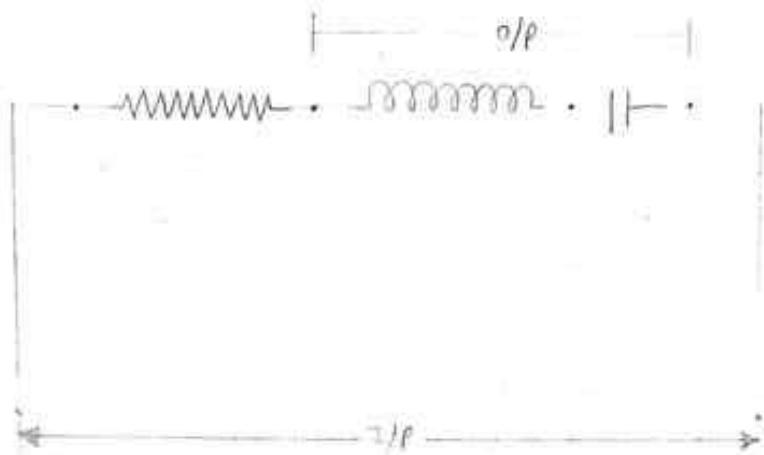

Impedance Curve  
for Series Resonance

AIM : To study series resonance circuits

APPARATUS : Function generator, CRO, series resonance kit

$R = 1 \text{ k}\Omega$ ,  $L = 39 \text{ mH}$ ,  $C = 0.1 \mu\text{F}$

SrNo	PRO 2	
	Series Resonant Frequency (kHz)	
1.	Observed	Calculated
	2.5485 Hz	2.5485 Hz

SrNo	PRO 3	
	Frequency (Hz)	V <sub>ref</sub>
1	100	2.55 V
2	500	2.112 mV
3	1000	9.00 mV
4	1200	2.119 V
5	1500	5.16 mV
6	2000	1.66 mV
7	2300	1.13 mV
8	2500	-1.59 mV
9	3000	-2.59 mV
10	4000	-1.56 mV

### CALCULATION:

$$Y_L = Y_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$


$$\frac{1}{2\pi^2 LC}$$



$$f = \frac{1}{2\pi \sqrt{LC}} = 2548.5$$

Scale

In X axis : 2 cm = 500 Hz

On Y axis : 2 cm = 1 V

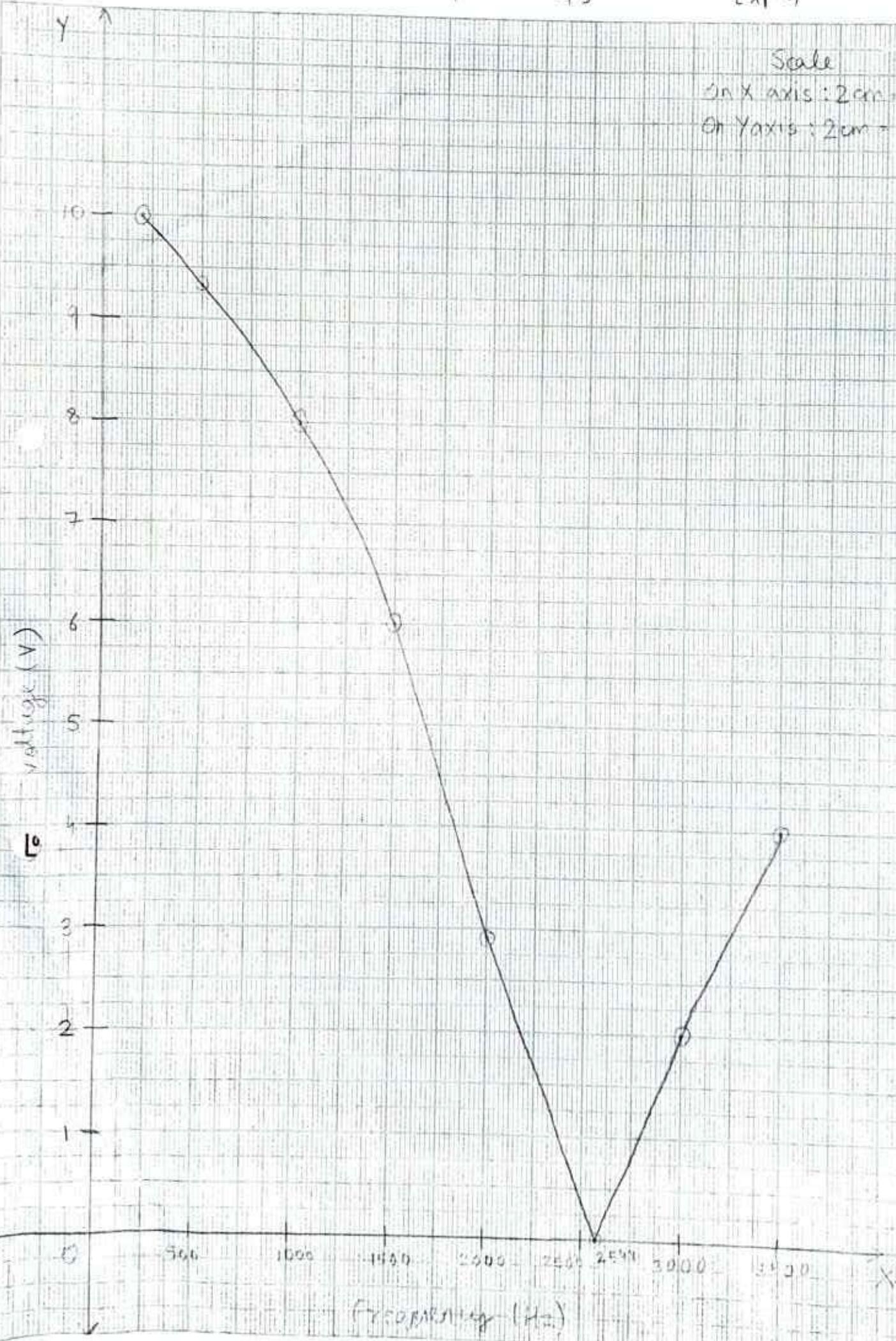

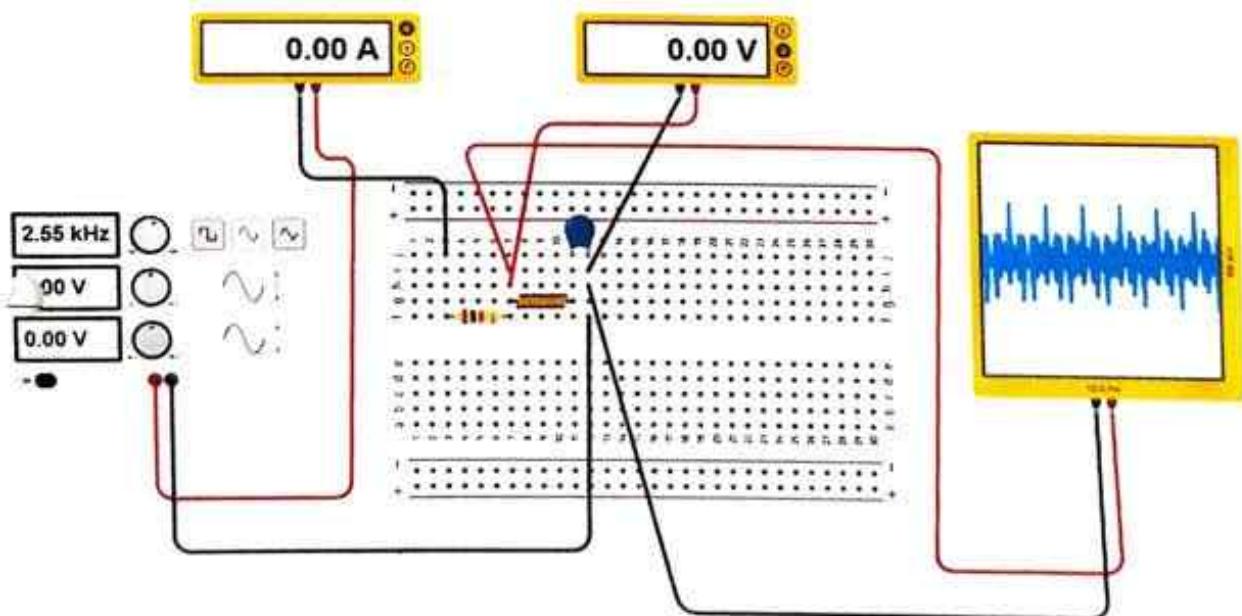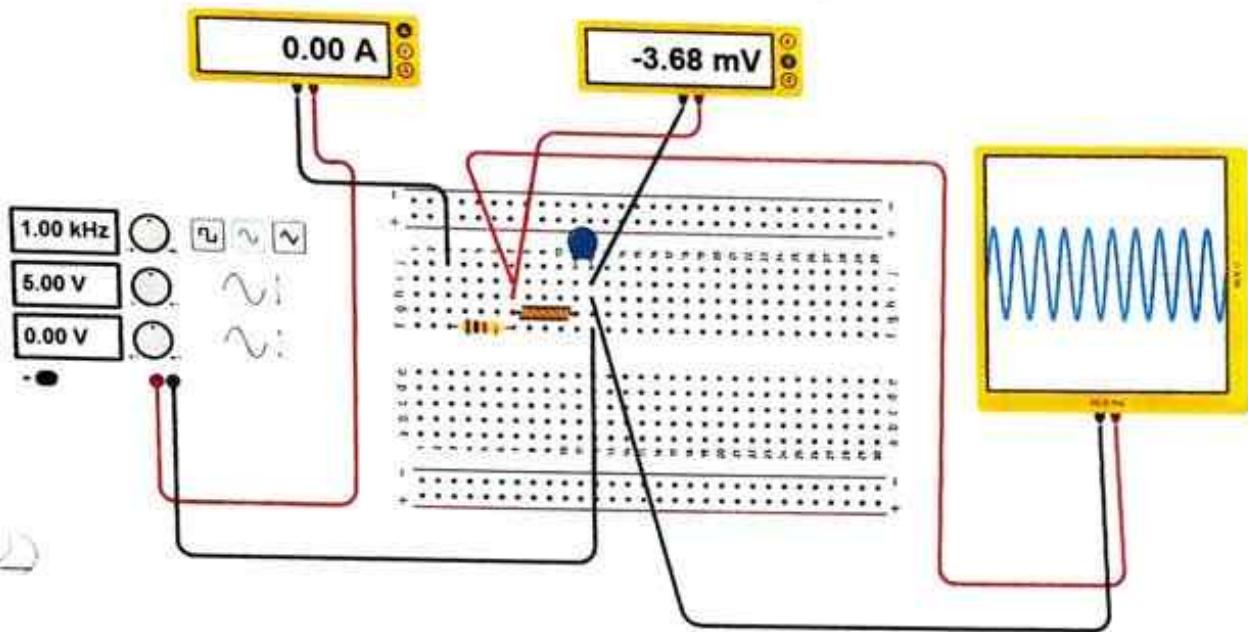

### RESULT AND DISCUSSION :

PRO 2: At series resonance frequency, the peak-to-peak voltage almost tends to zero to make the input AC signal appear a straight line.

PRO 3: The voltage across the inductor and capacitor is very high as compared to the input voltage, however the voltages are  $180^\circ$  out of phase with each other resulting in a total voltage drop of 0V at series resonant frequency.

CONCLUSION: Hence in series RLC circuit when AC signal of variable frequency is applied at low frequency ( $f < f_0$ ) circuit is capacitive in nature, at very high frequency ( $f > f_0$ ) circuit is inductive in nature. When  $X_L = X_C$ , resonance occurs and current in the circuit is maximum.

### QUIZ:

- 1] Derive the expression at series resonant frequency
- Imaginary term of impedance  $z$  is zero i.e. the value of  $X_L - X_C$  should be equal to zero  
 $\Rightarrow X_L = X_C$

$$\text{Substitute } X_L = 2\pi f L \text{ & } X_C = \frac{1}{2\pi f C}$$

$$\therefore 2\pi f L = \frac{1}{2\pi f C} \Rightarrow f^2 = \frac{1}{4\pi^2 LC} \Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

- 2] Draw the impedance curve for series resonance  
 → Refer Blank page.

Subject :- BEF

Experiment / Tutorial / Assignment No. :- 4

Page :- 4

Objective	PRO1	PRO2	PRO3		TOTAL	ES & H DEPARTMENT TCET
weight	20	30	30		SCORE	Date of Performance: 9/3/21
points						Date of correction:
SCORE						Roll No: 45
						Marks : /100

Earned Points (EP) = Total score / 60 Marks in 100 Signature of Faculty:  
= EP \* 20



Zaydu Singh Charitable Trust's (Regd.)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education (AICTE) and Government of Maharashtra (GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20

Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NERF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified • Programmes Accredited by National Board of Accreditation (NBA), New Delhi

\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

Ishika Sharma

FF - A1805

45

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 5

Page :- 1


Date :- 16 / 3 / 2021

## EXPERIMENT NO. 5


### TRANSFORMER EQUIVALENT CIRCUIT



FROM OC & SC TEST


\* CIRCUIT DIAGRAM FOR O.C TEST

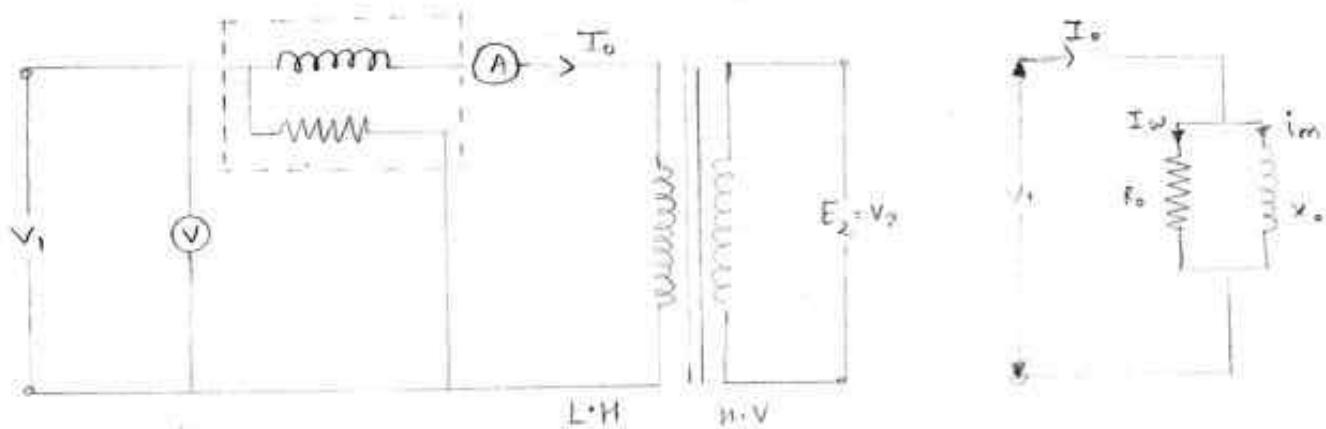

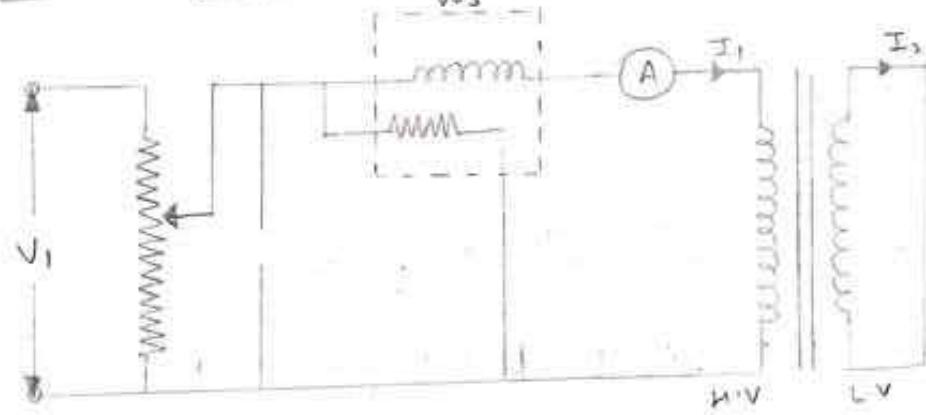\* CIRCUIT DIAGRAM FOR  $\frac{w_s}{w_s}$  SC TEST



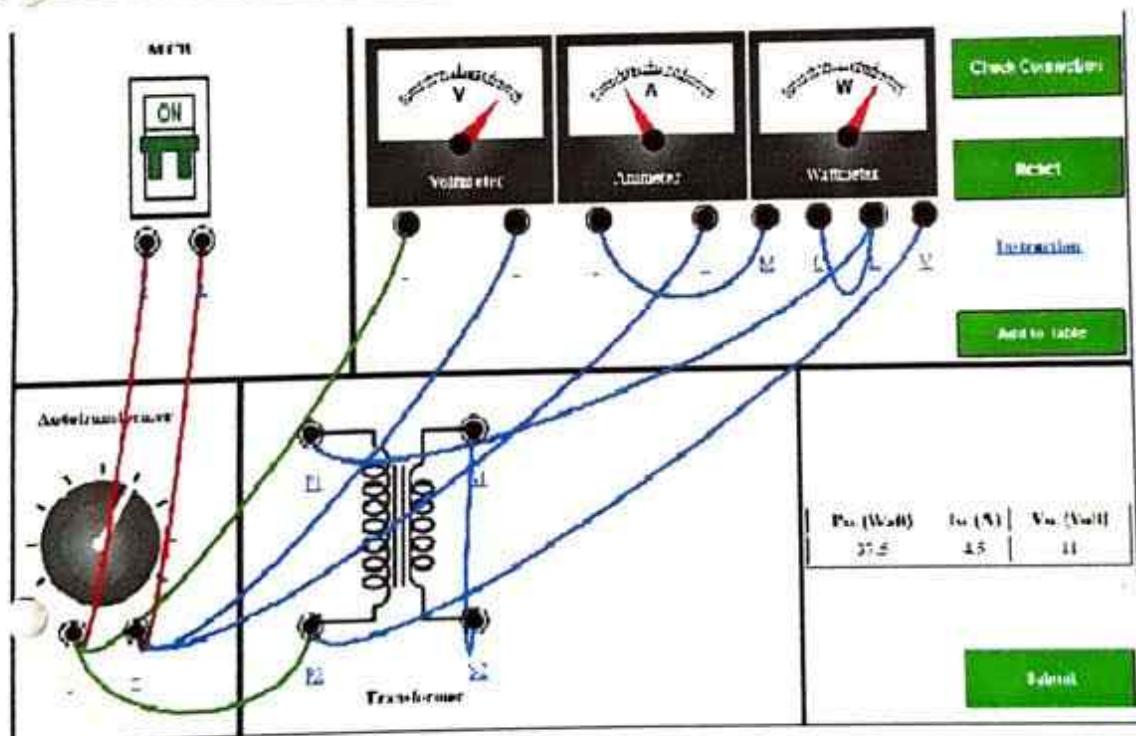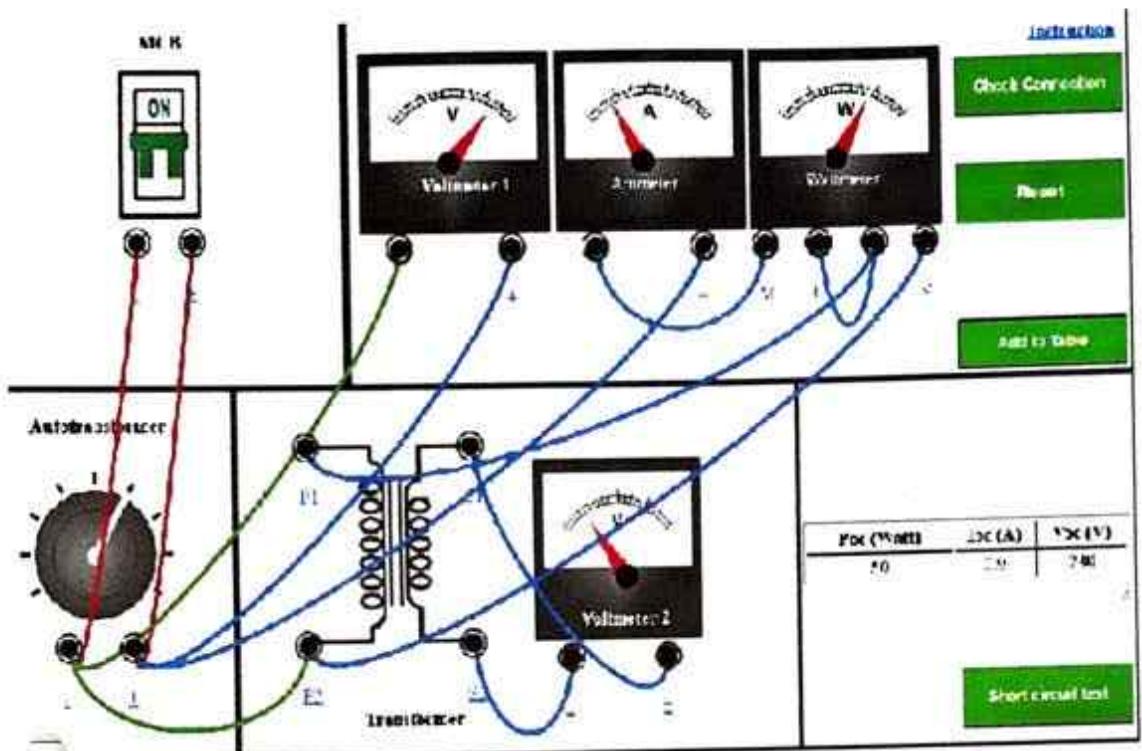

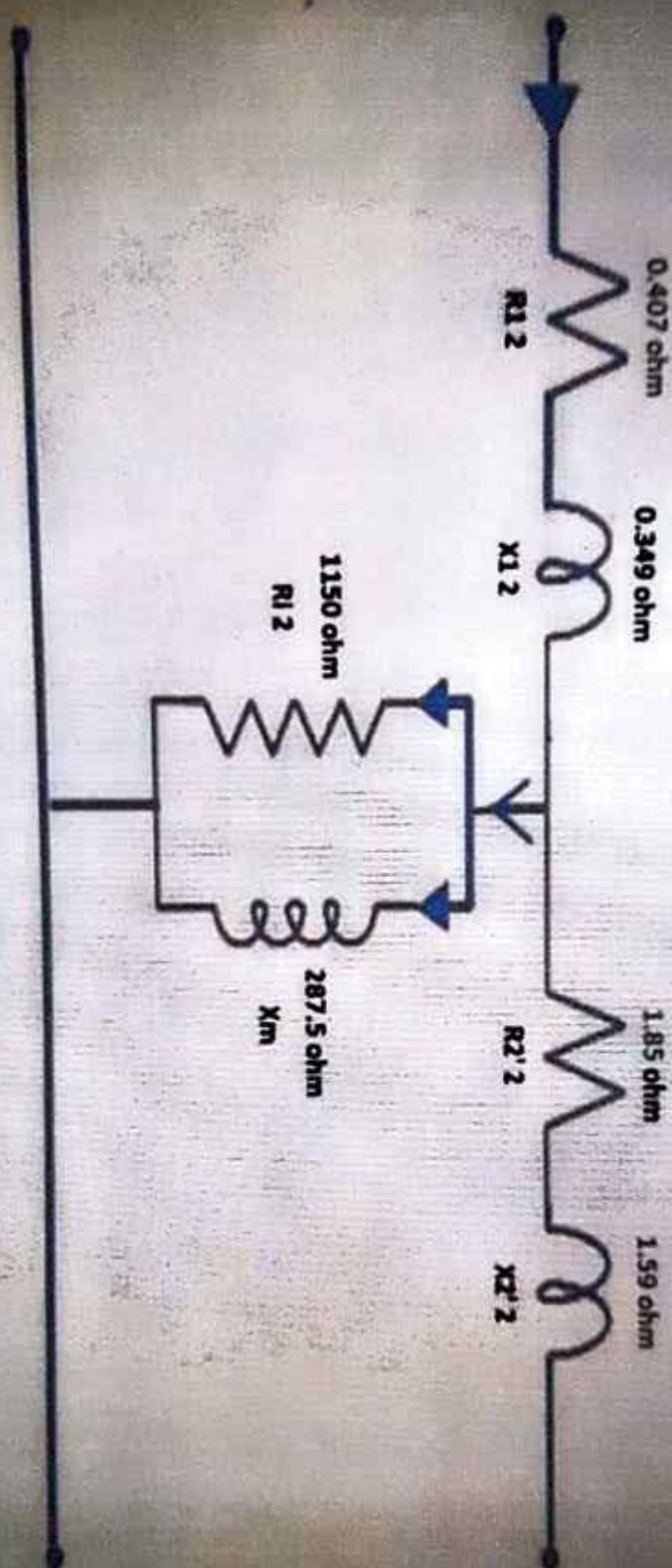

AIM : Determination of Transformer equivalent circuit from Open Circuit and Short Circuit Test

CONCLUSION: We have successfully determined transformer equivalent circuit from open circuit & close circuit. we performed the OC test to find the transformer equivalent.

Objective	PRO1	PRO2	PRO3	TOTAL	ES&H DEPARTMENT TCET
weight	20	20	20	SCORE	Date of Performance:
Points					Date of Correction:
<u>SCORE</u>					ROLL NO: <u>45</u>
Earned Points (EP)	Total Score	Marks in 100	Signature of Faculty:	Marks :	/100
	60	• EP * 20			



Zagdu Singh Charitable Trust's (Regd.)

Website : [www.tcetmumbai.in](http://www.tcetmumbai.in)

## THAKUR COLLEGE OF ENGINEERING & TECHNOLOGY

Autonomous College Affiliated to University of Mumbai

Approved by All India Council for Technical Education(AICTE) and Government of Maharashtra(GoM)

Conferred Autonomous Status by University Grants Commission (UGC) for 10 years w.e.f. A.Y 2019-20  
Amongst Top 200 Colleges in the Country, Ranked 193<sup>rd</sup> in NIRF India Ranking 2019 in Engineering College category

\* ISO 9001:2015 Certified \* Programmes Accredited by National Board of Accreditation (NBA), New Delhi  
\* Institute Accredited by National Assessment and Accreditation Council (NAAC), Bangalore

Ishika Sharma

FE - A I E D S

45

Subject :- BEF

Experiment / Tutorial / Assignment No. :- 6


Page :- 1


Date :- 18/3/2021

## EXPERIMENT NO. 6

### SLIPPING INDUCTION

MOTOR

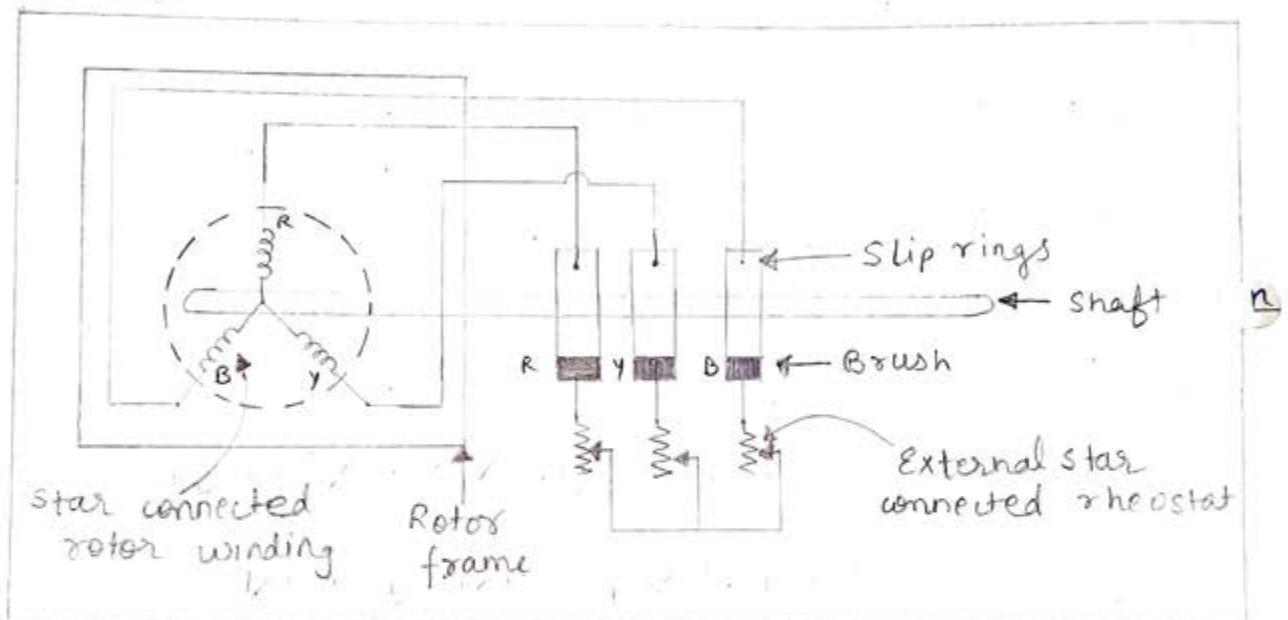

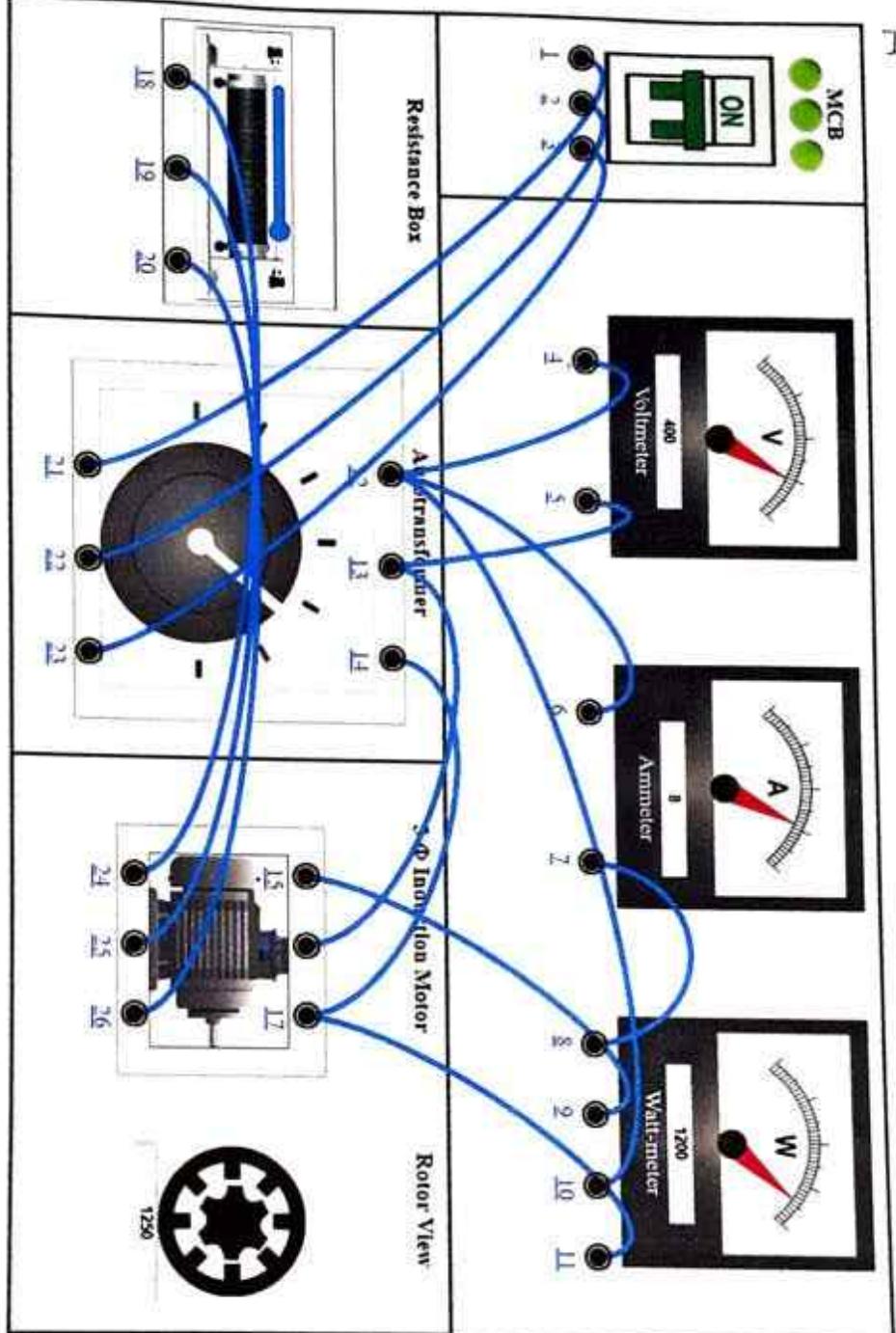

Resistance

35%  
3

SN	Ammeter	Wattmeter	Speed
1	2.6	40	1474
2	2.9	140	1454
3	4.8	680	1388
4	5.5	820	1363
5	6.1	940	1352
6	6.4	1040	1334
7	6.9	1100	1300
8	7.5	1160	1278
9	8	1200	1250

Print this page

Reset

Add to table

Graph

Instruction

AIM: Speed control of slipring Induction Motor

CONCLUSION: We got to learn about the slipring Induction motor and its speed control. We were also able to make proper connection and get the readings.

Objective	PRO1	PRO2	PRO3	TOTAL	ES&H DEPARTMENT - TCET
weight	20	20	20	SCORE	Date of Performance: 18/3/21
points					Date of Correction:
SCORE					Roll No: <u>45</u>
Earned Points (EP)	60	Total Score	Marks in 100 EP * 20		Marks : <u>/100</u>
					Signature of Faculty: _____

## TUTORIAL 1

Ishika Sharma  
FE-A19D3  
45

Subject - BEE


Experiment / Tutorial / Assignment No. - 1

Page :- 1

- Q1] Determine currents  $I_1$ ,  $I_2$  and  $I_3$  in Fig. given below. Also find power dissipated in each resistor.



sol:

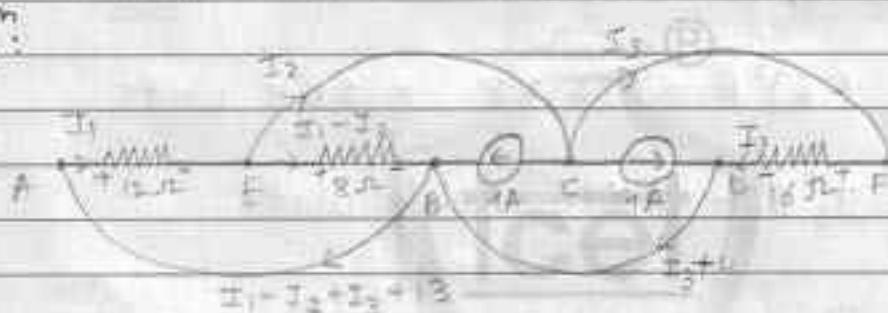

From fig.

$$I_1 = I_1 = I_2 + I_3 + 1A$$

$$I_2 = I_3 = 1A \quad \text{--- (1)}$$

Apply KVL in ABEA

$$-12I_1 - 8(I_1 - I_2) = 0$$

$$-12I_1 - 8I_1 + 8I_2 = 0$$

$$-20I_1 + 8I_2 = 0 \quad \text{--- (2)}$$

Apply KVL in AEFCFDBA

$$-12I_1 - 16I_3 = 0 \quad \text{--- (3)}$$

By solving - 1, 2 & 3

$$I_1 = 6 \text{ A}, \quad I_2 = 10 \text{ A}, \quad I_3 = -3 \text{ A}$$

Power dissipated

$$P_{12\Omega} = I_1^2 R = 16 \times 12 = 192 \text{ Watt}$$

$$P_{8\Omega} = (-6)^2 R = 36 \times 8 = 288 \text{ Watt}$$

$$P_{16\Omega} = I_3^2 R = 9 \times 16 = 144 \text{ Watt}$$

∴ Power dissipated through  $12\Omega$ ,  $8\Omega$  &  $16\Omega$  resistors are 192 Watt, 288 Watt & 144 Watt respectively.

Q2] Find the voltage of point A w.r.t. B, A is +ve w.r.t. B.



Sol:

In Loop 1,

$$\therefore I_1 = \frac{10}{5+3} = \frac{10}{8} = 1.25 \text{ A}$$

In second loop,

$$I_2 = 5 \text{ A}$$

Apply KVL from A to B

$$\therefore V_A - 3I_1 - 8 - 3(-I_2) - V_B = 0$$

$$V_{AB} - 3I_1 - 8 + 3I_2 - V_B = 0$$


$$V_{AB} - 3(1.25) - 8 + 3(5) = 0$$

$$V_{AB} + 3.25 = 0$$

$$\therefore V_{AB} = -3.25 \text{ V}$$

$\therefore$  voltage of point A w.r.t. B is -3.25 V

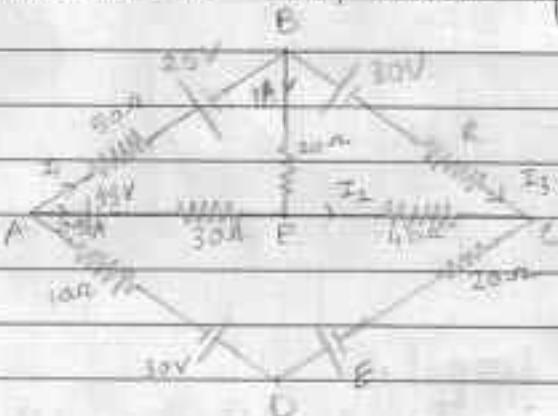Q3) For the network shown below determine i)  $I_1, I_2, I_3$   
ii) Resistance  $R$  iii) Value of EMF E.



Sol<sup>n</sup>: Apply KVL in loop ABEA,

$$-50I_1 - 25 - 20I_1 - 30(-0.5) + 45 = 0$$

$$-50I_1 - 25 - 20 + 15 + 45 = 0$$

$$-50I_1 + 15 = 0$$

$$I_1 = \frac{15}{50}$$

$$\underline{\underline{I_1 = 0.3 \text{ A}}}$$

Now,

$$I_2 = 1 + 0.5 \\ \underline{\underline{I_2 = 1.5 \text{ A}}}$$

$$I_1 = 1 + I_3 \\ 0.3 = 1 + I_3 \\ \underline{\underline{I_3 = -0.7 \text{ A}}}$$

Apply KVL in loop EBCE

$$-20(I_1) - 30 - R(I_3) - 40(-I_2) = 0$$

$$20 - 30 - R(-0.7) - 40(-1.5) = 0$$

$$D. 7R + 50 = 0$$

$$R = -\frac{50}{0.7} = -71.43$$

But, Resistance cannot be negative  
 $\therefore R = \underline{71.43 \Omega}$

Apply KVL in loop AECD<sub>A</sub>,

$$-45 - 30(0.5) + v_0(1.5) - 20(I_3 + I_2) + E - 30 - 10(I_3 + I_2) = 0$$

$$-45 - 15 - 60 - 20(0.7 + 1.5) + E - 30 - 10(-0.7 + 1.5) = 0$$

$$E = 174$$


$$\therefore E = \underline{174 \text{ V}}$$

$$\therefore I_1 = 0.3 \text{ A}, I_2 = 1.5 \text{ A}, I_3 = -0.7 \text{ A}$$


$$R = \underline{71.43 \Omega}$$

$$E = \underline{174 \text{ V}}$$

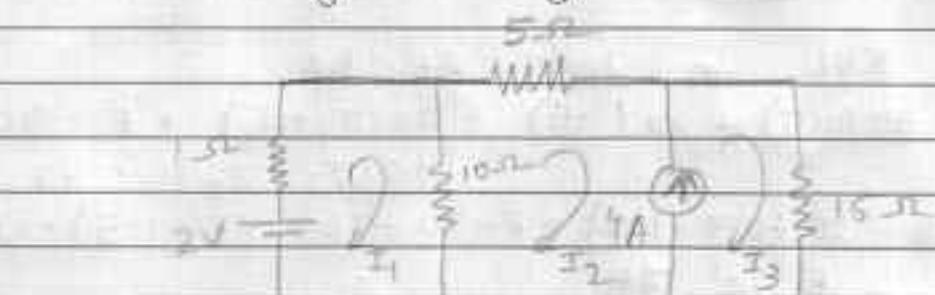Q4) Find current through  $10\ \Omega$  resistor using mesh analysis.



Sol<sup>n</sup>:

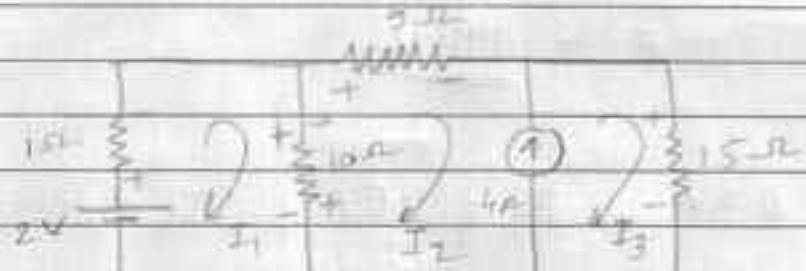

Writing current eq<sup>n</sup> for supermesh

$$I_3 - I_2 = 4 \quad \left. \begin{array}{l} \text{Direction of } I_3 \text{ is} \\ \text{same} \end{array} \right\}$$

$$0I_1 - I_2 + I_3 = 4 \quad \text{---(1)}$$

Writing KVL eq<sup>n</sup> for outerloop of supermesh

$$-5I_2 - 15I_3 - 10(I_2 - I_1) = 0$$

$$-5I_2 - 15I_3 - 10I_2 + 10I_1 = 0$$

$$10I_1 - 15I_2 - 15I_3 = 0 \quad \text{---(2)}$$

Apply KVL in mesh 1,

$$-10(I_1 - I_2) + 2 - I_1 = 0$$

$$-10I_1 + 10I_2 + 2 - I_1 = 0$$

$$-11I_1 + 10I_2 + 0I_3 = -2 \quad \text{---(3)}$$

solving eq<sup>n</sup> 1, 2 & 3


$$I_1 = -2.35\ A, I_2 = -2.78\ A, I_3 = 1.22\ A$$

$\therefore$  current through  $10\ \Omega$  is


$$I_{10\Omega} = I_1 - I_2 = -2.35 + 2.78 = 0.43\ A$$

$\therefore$  current through  $10\ \Omega$  is  $0.43\ A$ .

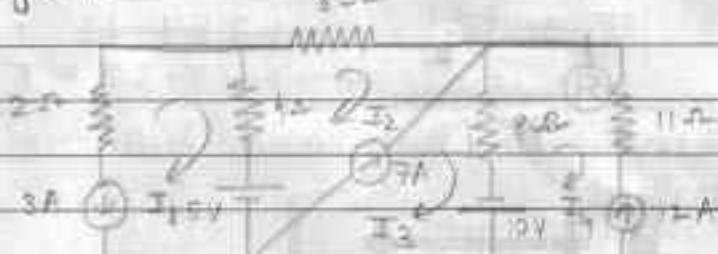Q5) Find current through  $4\ \Omega$  resistor using mesh analysis.



Sol<sup>n</sup>:

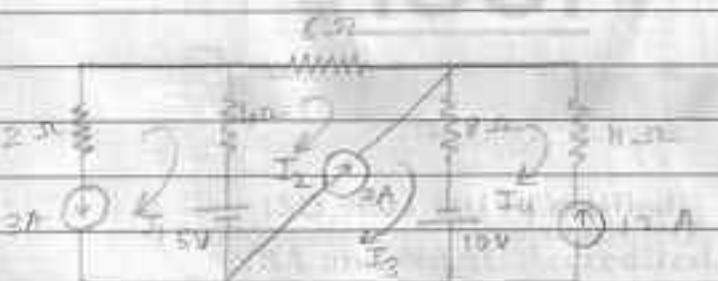

Here, mesh 2 & 3 form supermesh,

$\therefore$  current eq<sup>n</sup> for supermesh,

$$I_3 - I_2 = 7 \\ 0I_1 - I_2 + I_3 = 7 \quad \text{---(1)}$$

$\because$  Mesh 1 & mesh 4 contains current source

$$\therefore I_1 = -3\ A, \quad I_4 = -12\ A$$

Apply KVL in the outer loop of the supermesh,

$$-6I_2 - 8(I_3 - I_4) + 10 + 5 - 4(I_2 - I_1) = 0$$

$$-6I_2 - 8I_3 + 8I_4 + 15 - 4I_2 + 4I_1 = 0$$

$$-12 - 10I_2 - 8I_3 - 96 = -15$$

$$-10I_2 - 8I_3 = 93 \quad \text{---(2)}$$

Solving eq<sup>n</sup> ① & ②


$$I_2 = -8.28 \text{ A} \quad , \quad I_3 = -1.28 \text{ A}$$

∴ current through  $4\Omega$ -resistor


$$\therefore I_{8\Omega} = I_1 - I_2 = -1.28 + 12 = 10.72 \text{ A}$$

$$= -3 + 8.28 = 5.28 \text{ A}$$

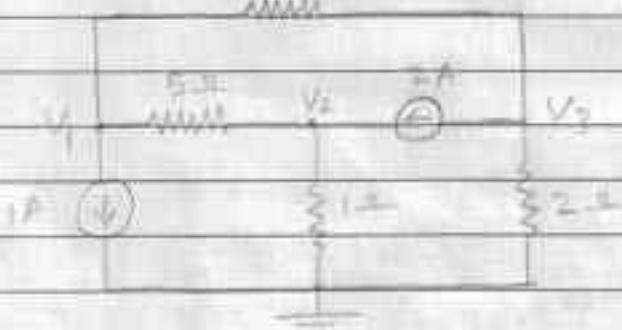Q6] Find current in  $1\Omega$ -resistor and  $4\Omega$ -resistor using nodal analysis



Sol:

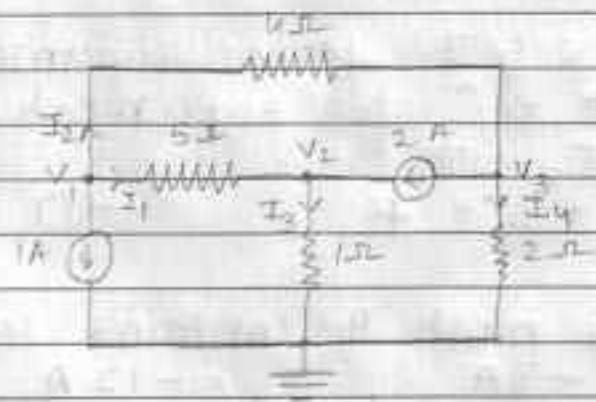

Apply KCL at node 1

$$I + I_1 + I_2 = 0$$

$$\frac{V_1 - V_2}{5} + \frac{V_1 - V_3}{4} = -1$$

$$0.2V_1 - 0.2V_2 + 0.25V_1 - 0.25V_3 = -1$$

$$0.45V_1 - 0.2V_2 - 0.25V_3 = -1 \quad \text{--- (1)}$$

Apply KCL at node 2,

$$I_1 + 2 = I_3$$

$$\frac{V_1 - V_2}{5} + \frac{V_2 - 0}{1} = -2$$

$$0.2V_1 - 0.2V_2 - V_2 = -2$$

$$0.2V_1 - 1.2V_2 = -2 \quad \text{--- (2)}$$

Apply KCL at node 3,

$$I_2 = 2 + I_4$$

$$\frac{V_1 - V_3}{4} = 2 + \frac{V_3 - 0}{2}$$

$$0.25V_1 - 0.25V_3 = 2 + 0.5V_3$$

$$0.25V_1 - 0.75V_3 = 2 \quad \text{--- (3)}$$

On solving 1, 2, 3

$$V_1 = -4V, V_2 = 1V, V_3 = -4V$$

$$\text{Current through } 1\Omega (I_{in}) = I_3 = \frac{V_2}{1} = 1A,$$

$$\text{Current through } 4\Omega (I_{out}) = \frac{V_1 - V_3}{4} = \frac{-4 - 4}{4} = 0A$$

# TUTORIAL 2


Ishika Sharma  
FE-AI & DS  
45

Subject - BEE


Experiment / Tutorial / Assignment No. - 2

Page - 1

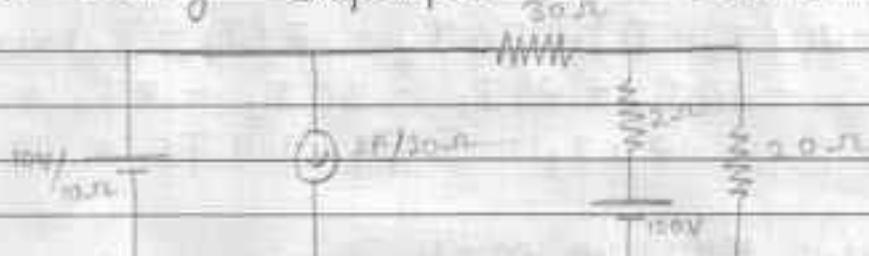
Q1] For given circuit find current through  $30\Omega$  resistor using superposition theorem



Sol:

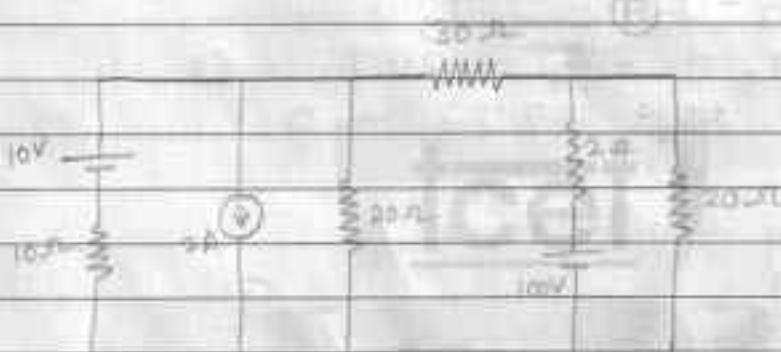

Case 1: when 10V is acting alone

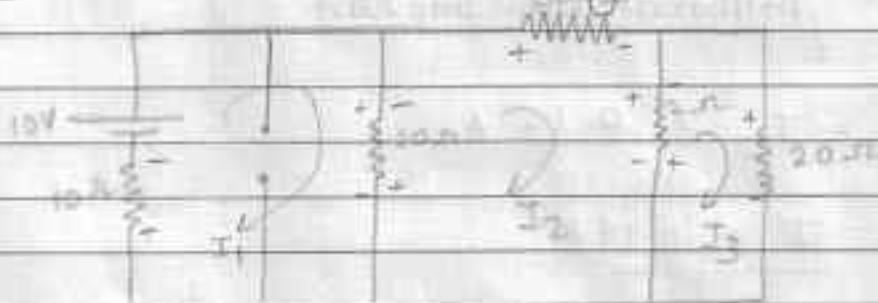

Apply KVL in mesh 1,

$$10 - 20(I_1 - I_2) - 10I_1 = 0$$

$$10 - 20I_1 + 20I_2 - 10I_1 = 0$$

$$-30I_1 + 20I_2 = -10 \quad \text{--- (1)}$$

Apply KVL in mesh 2,

$$-20(I_2 - I_1) - 30I_2 - 2(I_1 - I_3) = 0$$

$$-20I_2 + 20I_1 - 30I_2 - 2I_1 + 2I_3 = 0$$

$$\therefore 20I_1 - 52I_2 + 2I_3 = 0 \quad \text{--- (2)}$$

Apply KVL in mesh 3,

$$-2(I_2 - I_3) - 20I_3 = 0$$

$$-2I_3 + 2I_2 - 20I_3 = 0$$

$$2I_2 - 23I_3 = 0 \quad \text{--- (3)}$$

Solving eq<sup>n</sup> 1, 2, 3

$$I_1 = 0.45 \text{ A}$$


$$I_2 = 0.17 \text{ A}$$

$$I_3 = 0.015 \text{ A}$$

$$\therefore I' = I_2 = 0.17 \text{ A}$$


$$\underline{I' = 0.17 \text{ A}}$$

Case 2 when 2A is acting alone.

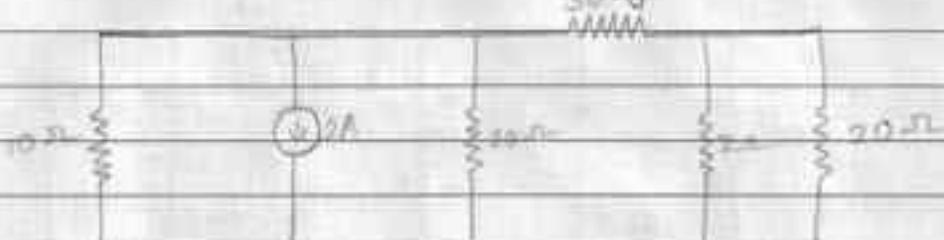

∴ Resistors  $5\Omega$  &  $20\Omega$  are parallel
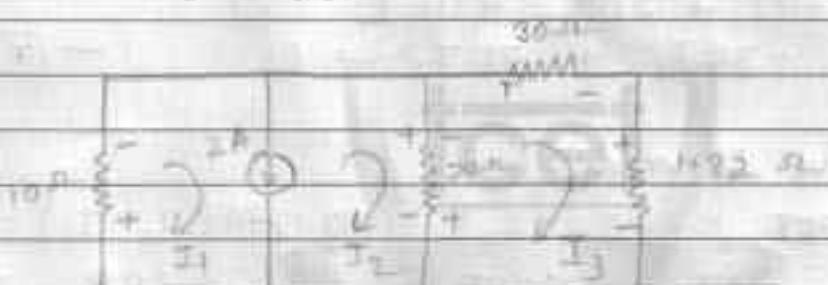
$$\frac{1}{5} + \frac{1}{20} = \underline{1.82\Omega}$$



Apply KVL over mesh 1 & 2

$$-10I_1 - 20(I_2 - I_3) = 0$$

$$-10I_1 - 20I_2 + 20I_3 = 0 \quad -④$$

Apply KVL in mesh 3,

$$-20(I_3 - I_2) - 30I_3 - 1.82I_3 = 0$$

$$-20I_3 + 20I_2 - 30I_3 - 1.82I_3 = 0$$

$$\therefore 20I_2 - 51.82I_3 = 0 \quad -⑤$$

Apply super mesh condition in mesh 1 & 2

$$I_1 - I_2 = 2 \quad -⑥$$

By solving 4, 5, 6

$$I_1 = 1.1 \text{ A}, I_2 = -0.89 \text{ A}, I_3 = -0.346 \text{ A}$$

$$\therefore I'' = I_3 = \underline{-0.346 \text{ A}}$$

Case 3: when 100 V is acting alone.



Apply KVL in mesh 1,

$$-20(I_1 - I_2) - 10I_1 = 0$$

$$-20I_1 + 20I_2 - 10I_1 = 0$$

$$-30I_1 + 20I_2 = 0 \quad \text{--- (1)}$$

Apply KVL in mesh 2,

$$-30I_2 - 2(I_2 - I_3) - 100 - 20(I_3 - I_1) = 0$$

$$-32I_2 + 2I_3 + 2I_1 = 100 \quad \text{--- (2)}$$

Apply KVL in mesh 3,

$$100 - 2(I_3 - I_2) - 20I_3 = 0$$

$$2I_2 - 22I_3 = -100 \quad \text{--- (3)}$$

On solving 1, 2, 3

$$I_1 = -1.57 \text{ A}, \quad I_2 = -2.36 \text{ A}, \quad I_3 = 4.33 \text{ A}$$

$$\therefore I'' = I_2 = -2.36 \text{ A}$$

∴ current through  $30 \Omega$ ,


$$I_{30\Omega} = I' + I'' + I'''$$

$$= 0.17 + 0.346 - 2.36$$


$$= -2.54 \text{ A}$$

∴ current through  $30 \Omega$  is  $-2.54 \text{ A}$

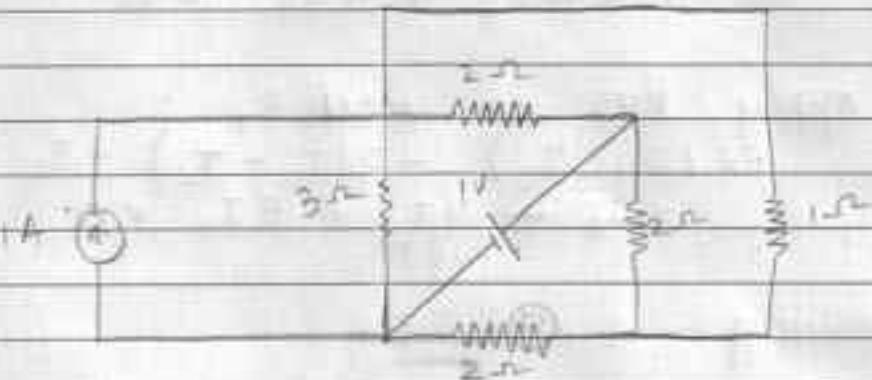Q2] Find the current through  $1\Omega$  resistor using superposition theorem.



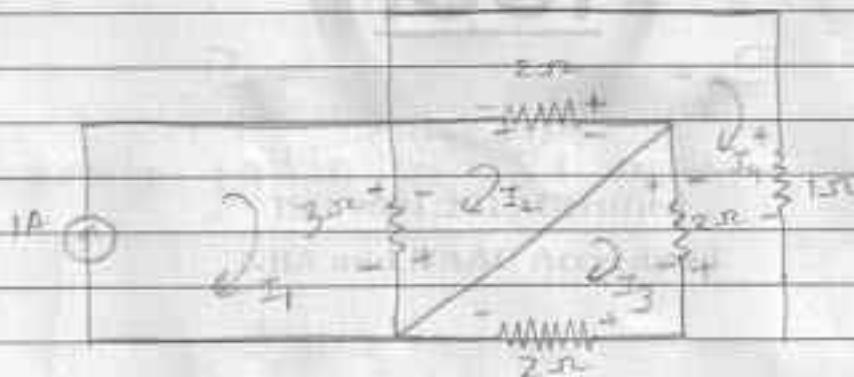Sol<sup>n</sup>: When 1A is acting alone,



$\therefore$  Mesh 1 contains a current source  
 $I_1 = 1A$  q. Direction is same?

Apply KVL in mesh 2,

$$-2(I_2 - I_4) - 3(I_2 - I_1) = 0$$

$$-2I_2 + 2I_4 - 3I_2 + 3I_1 = 0$$

$$-5I_2 + 2I_4 = -3 \quad \text{--- (1)}$$

Apply KVL in mesh 3,

$$-2(I_3 - I_4) - 2I_3 = 0$$

$$-4I_3 + 2I_4 = 0$$

- (2)

Apply KVL in mesh 4,

$$-2(I_4 - I_3) - 2(I_4 - I_2) - I_4 = 0$$

$$2I_2 + 2I_3 - 5I_4 = 0$$


- (3)

solving 1, 2, 3

$$I_2 = 0.75A, \quad I_3 = 0.18A, \quad I_4 = 0.375A$$

$$\therefore I' = I_1 = \underline{0.375A}$$

Case 2: when 1V in acting alone

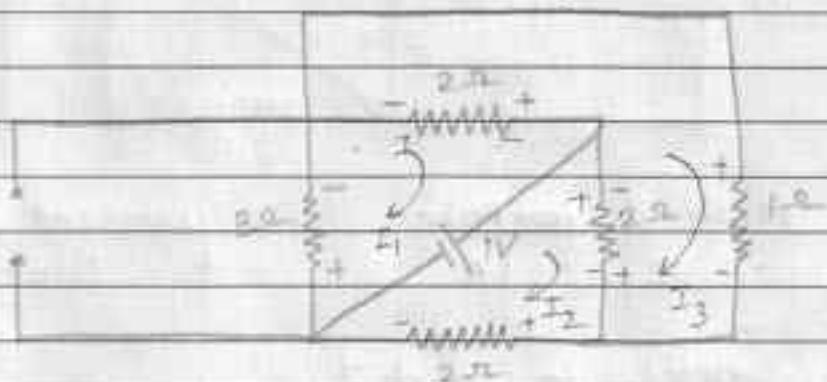

Apply KVL in mesh 2,

$$-3I_1 - 2(I_1 - I_3) - 1 = 0$$

$$-3I_1 - 2I_1 + 2I_3 - 1 = 0$$

$$-5I_1 + 2I_3 = 1$$

- (4)

Apply KVL in mesh 2,

$$1 - 2(I_2 - I_3) - 2I_2 = 0$$

$$-4I_2 + 2I_3 = -1 \quad \text{--- (5)}$$

Apply KVL in mesh 3,

$$-2(I_3 - I_2) - 2(I_3 - I_1) - I_3 = 0$$

$$-2I_3 + 2I_2 - 2I_3 + 2I_1 - I_3 = 0$$

$$2I_1 + 2I_2 - 5I_3 = 0 \quad \text{--- (6)}$$

On solving 4, 5, 6

$$I_1 = 0.18A, \quad I_2 = 0.26A, \quad I_3 = 0.031A$$

$$\therefore I' + I_3 = 0.031A$$

Current flowing through  $1\Omega$  is

$$I_{1\Omega} = I' + I_3$$

$$= 0.375 + 0.031$$


$$= 0.406A$$

$\therefore$  current through  $1\Omega$  is 0.406A

Q3] Find the current through  $30\Omega$  resistor using Thevenins Theorem



Sol:

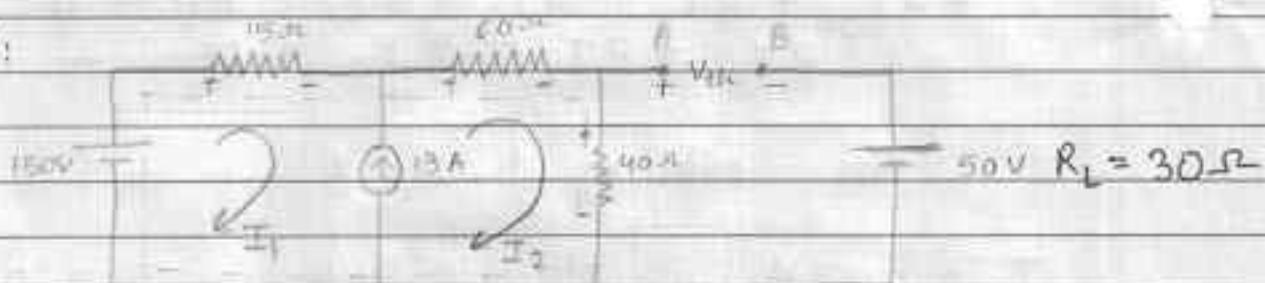

Apply KVL in mesh +

writing current eq<sup>n</sup> for supermesh

$$-15I_1 + I_2 - I_1 = 13 \quad i.e. \text{ the direction of } I_2 \\ I_1 - I_2 + 0I_3 = -13 - (1) \text{ and source is same?}$$

Writing KVL eq<sup>n</sup> for outer loop of supermesh

$$-15I_1 - 60I_2 - 40I_2 + 150 = 0$$

$$-15I_1 - 100I_2 = -150$$

$$15I_1 + 100I_2 + 0I_3 = 150 - (2)$$

Solving eq<sup>n</sup> 1 & 2

$$I_1 = -10A, I_2 = 3A$$


Writing  $V_{th}$  eq<sup>n</sup>

$$-50 + 40I_2 - V_{th} = 0$$

$$-50 + 120 - V_{th} = 0$$

$$V_{th} = 70 \text{ V}$$

Calculating  $R_{th}$ :

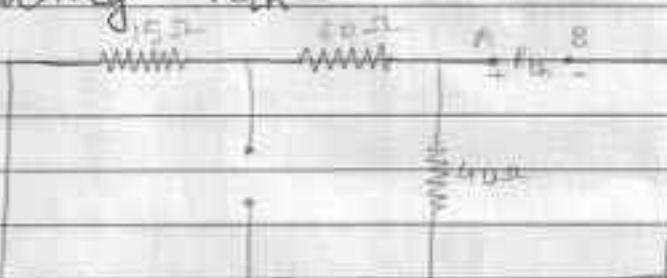

∴ Resistors 15 ohm & 60 ohm are in series  
 $\therefore 15 + 60 = 75 \text{ ohm}$



∴ Resistors 75 ohm & 40 ohm are in parallel

$$\frac{1}{75} + \frac{1}{40} = 26.08 \text{ ohm}$$

$$\therefore R_{th} = 26.08 \text{ ohm}$$


calculating  $I_L$ :

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{70}{26.08 + 30} = 1.25 \text{ A}$$




∴ current through 30 ohm is 1.25 A

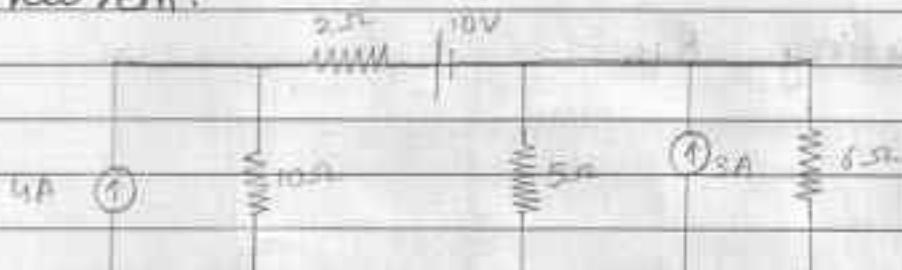Q4] Find current through  $6\Omega$  resistor using Thvenins Theorem.



Sol:

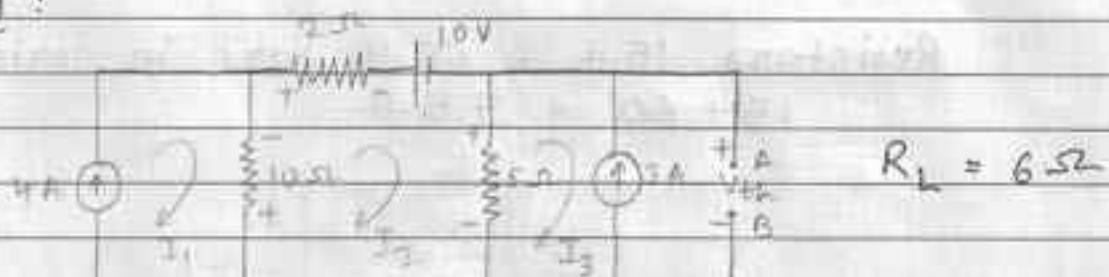

$\therefore$  mesh 1 & mesh 3 are containing current source

$$\begin{aligned} \therefore I_1 &= 4 \text{ A} & \{ \text{Direction is same} \} \\ \therefore I_3 &= -3 \text{ A} & \{ \text{Direction is opposite} \} \end{aligned}$$

Apply KVL in mesh 2,

$$\begin{aligned} -2I_2 - 10 - 5(I_2 - I_3) - 10(I_2 - I_1) &= 0 \\ -2I_2 - 10 - 5I_2 + 5I_3 - 10I_2 + 10I_1 &= 0 \\ 10I_1 - 17I_2 + 5I_3 - 10 &= 0 \\ 10 \times 4 - 17I_2 + 5(-3) - 10 &= 0 \\ 40 - 17I_2 - 15 - 10 &= 0 \\ -17I_2 &= -15 \\ I_2 &= \frac{15}{17} \\ I_2 &= 0.88 \text{ A} \end{aligned}$$

Writing  $V_{th}$  eq<sup>n</sup>

$$-V_{th} + 5(I_3 - I_2) = 0$$

$$-V_{th} + 5I_3 - 5I_2 = 0$$

$$-V_{th} + -15 - 4.4 = 0$$

$$-V_{th} - 19.4 = 0$$

$$V_{th} = -19.4 \text{ V}$$

$V_{th} = -19.4 \text{ V}$  (B is positive w.r.t A)

Calculating  $R_{th}$ :



∴ Resistors  $2\Omega$  &  $10\Omega$  are in series

$$\therefore 10 + 2 = 12\Omega$$




∴ Resistors  $12\Omega$  &  $5\Omega$  are parallel

$$\therefore \frac{1}{12} + \frac{1}{5} = 3.53 \Omega$$

$$\therefore R_{th} = 3.53 \Omega$$


Calculating  $I_L$

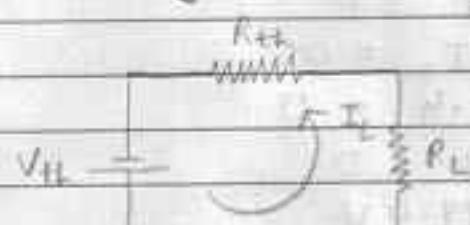


$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{19.4}{3.53 + 6} = 2.04 \text{ A}$$

$\therefore$  current through  $6\Omega$  is 2.04 A

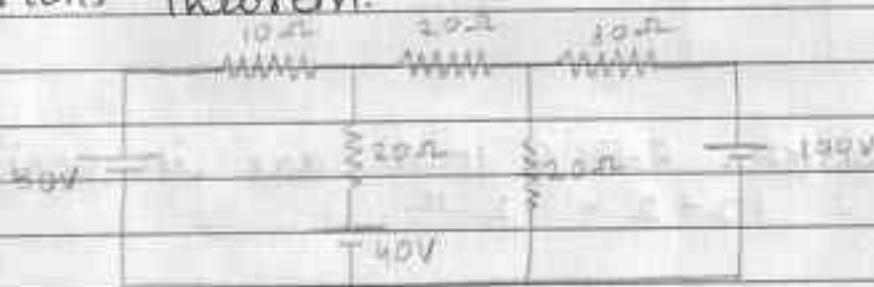Q5] Find current through  $10\Omega$  resistors using Norton's Theorem.



Sol": Calculating  $R_N$

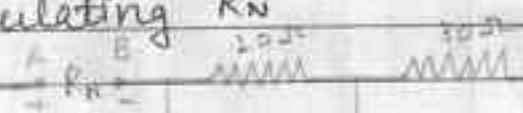

$$R_N = R_L = 10\Omega$$


$\therefore$  Resistors  $30\Omega$  &  $20\Omega$  are parallel

$$\frac{1}{30} + \frac{1}{20} = 12\Omega$$



∴ Resistors  $20\ \Omega$  &  $12\ \Omega$  are in series

$$\therefore 20 + 12 = 32\ \Omega$$

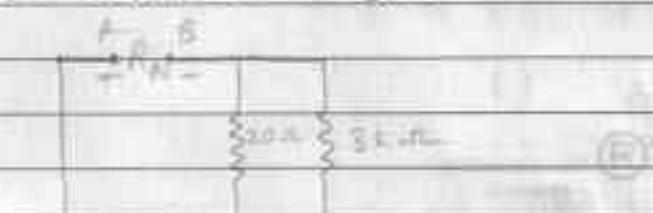

∴ Resistors  $20\ \Omega$  &  $32\ \Omega$  are parallel

$$\therefore \frac{1}{20} + \frac{1}{32} = 12.30\ \Omega$$

$$\therefore R_N = 12.3\ \Omega$$

Calculating  $I_N$



Apply KVL in mesh 1,

$$50 - 20(I_1 - I_2) - 40 = 0$$

$$50 - 20I_1 + 20I_2 - 40 = 0$$

$$-20I_1 + 20I_2 = -10 \quad \text{---(1)}$$

Apply KVL in mesh 2,

$$-20I_2 - 20(I_2 - I_3) + 40 - 20(I_2 - I_1) = 0$$

$$-20I_2 - 20I_2 + 20I_3 + 40 - 20I_2 + 20I_1 = 0$$

$$20I_1 - 60I_2 + 20I_3 = -40 \quad \text{---(2)}$$

Apply KVL in mesh 3,

$$-30I_3 - 100 - 20(I_3 - I_2) = 0$$

$$-30I_3 - 100 - 20I_3 + 20I_2 = 0$$

$$00I_2 - 50I_3 = 100 \quad \text{--- (3)}$$

On solving eq 1, 2 & 3


$$I_1 = 0.8125 \text{ A}$$

$$I_2 = 0.3125 \text{ A}$$

$$I_3 = -1.875 \text{ A}$$

$$I_N = I_1 = \underline{0.812} \text{ A}$$

2)

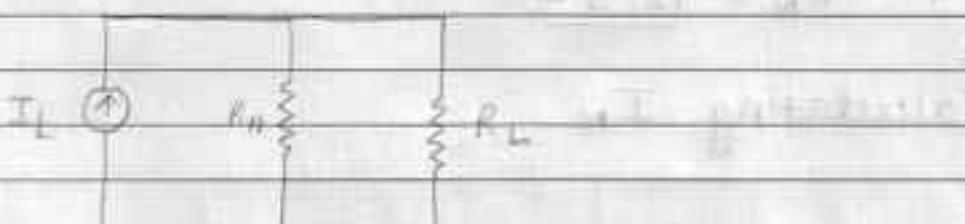

$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$

$$= \frac{12.3}{12.3 + 10} \times 0.812$$

$$I_L = 0.448 \text{ A}$$

∴ current through  $10\Omega$  is  $\underline{0.448} \text{ A}$

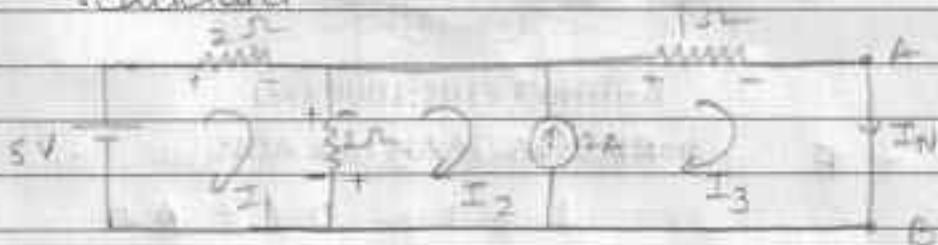
Q6] Find Norton's Equivalent network



Sol<sup>n</sup>: calculating  $I_N$  by joining A & B points



Here, 2Ω resistors are in parallel with 5V, so it is redundant



Apply KVL in mesh 1,

$$5 - 2I_1 - 2(I_1 - I_2) = 0$$

$$5 - 3I_1 + I_2 = -5 \quad \text{--- (1)}$$

Apply KVL in mesh 2 & 3,

$$-1I_3 - 2(I_2 - I_1) = 0$$

$$2I_1 - 2I_2 - I_3 = 0 \quad \text{--- (2)}$$

writing current eq<sup>n</sup> of supernode,


$$I_3 - I_2 = 2 \quad \text{--- (3)}$$

$\therefore$  On solving 1, 2, 3

$$I_1 = 1.86 \text{ A}, I_2 = 0.57 \text{ A}, I_3 = 2.57 \text{ A}$$

$$\therefore I_N = I_3 = \underline{\underline{2.57 \text{ A}}}$$

Calculating  $R_N$

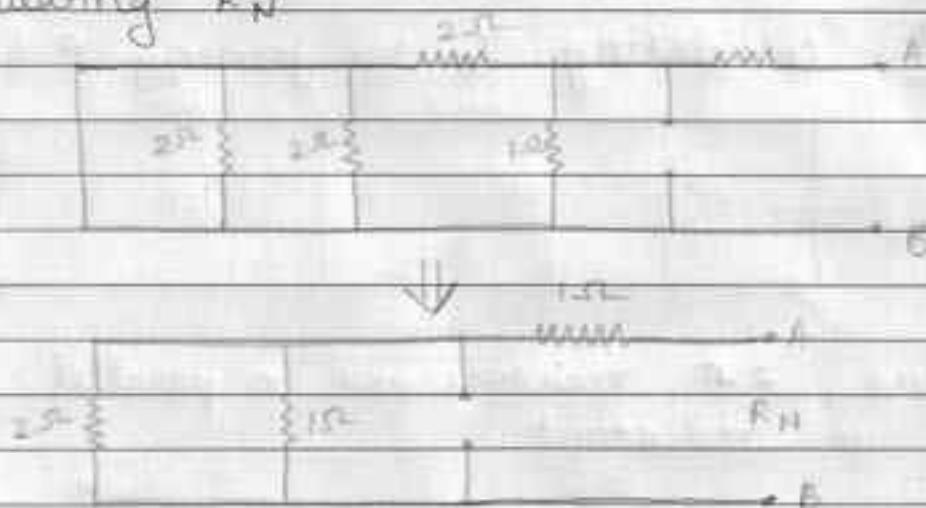


$\because$  Resistors 2Ω & 1.5Ω are parallel

$$\therefore \frac{1}{2} + 1 = 0.67 \Omega$$

$$\therefore R_N = 1 + 0.67 = \underline{\underline{1.67 \Omega}}$$

Norton's Equivalent network,

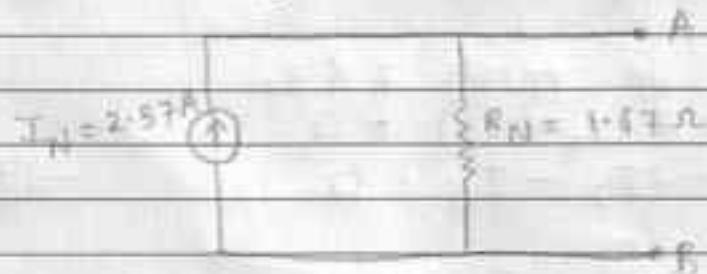

TUTORIAL 3


45

Subject:- BEE

Experiment / Tutorial / Assignment No. -&gt; 3

Page - 1

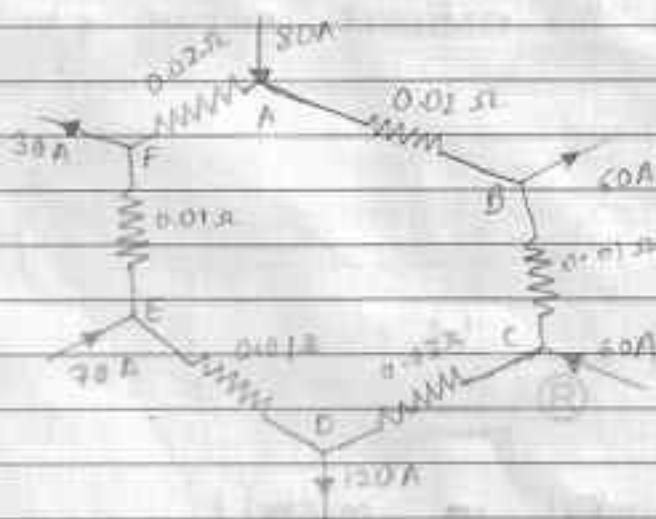Q1] Find currents in all the branches of the network shown



Sol:- Let current in branch  $AFA$  be  $I \rightarrow$   
 $\therefore$  current in  $AB$  is  $(I + 80) \rightarrow$

i. Applying KVL,

$$0.02I + 0.02(I+80) + 0.01(I+20) + 0.03(I+80)$$

$$0.01(I-40) + 0.01(I+30) = 0$$

$$0.01I - 0.4 + 0.01I + 0.3 = 0$$

$$0.1I + 4.1 = 0$$

$$I_{FA} = I = -41A$$

$$I_{BA} = I + 80 = 39A$$

$$I_{BD} = I + 20 = -21A$$

$$I_{CD} = I + 80 = 39A$$

$$I_{DE} = I - 40 = -81A$$


$$I_{EF} = I + 30 = -11A$$

$$\therefore I_{AB} = 39A, I_{BD} = -21A, I_{CD} = 39A, I_{DE} = -81A,$$

$$I_{EF} = -11A, I_{FA} = 41A$$

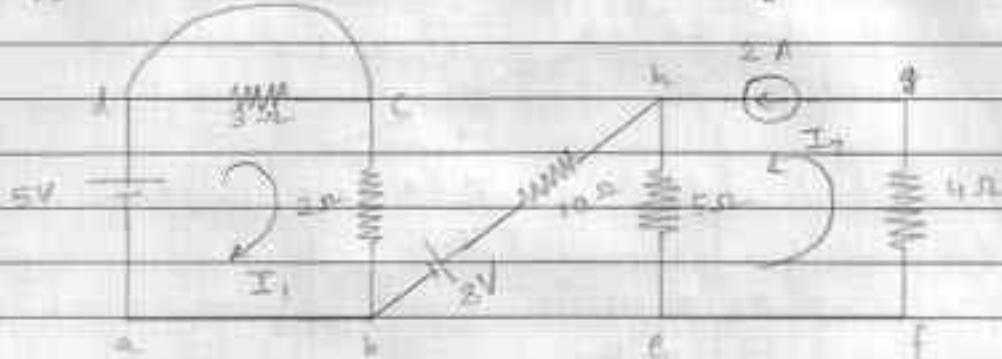Q3]

Find the potential at point e with respect to c ( $V_{ce}$ ) in the network shown below



Sol:

Apply KVL in mesh 1,

$$5V - 2\Omega \cdot I_1 + 5 = 0$$

$$I_1 = \underline{2.5 \text{ A}}$$

Also current in mesh 2 is  $I_2 = \underline{2 \text{ A}}$

Now Applying KVL from node e to e


$$V_c - 2I_1 + 8 - 10(0) - 5I_2 - V_e = 0$$

$$V_{ce} - 2(2.5) - 5(2) + 8 = 0$$

$$V_{ce} = \underline{7V}$$

The potential at point e w.r.t. c ( $V_{ce}$ ) is 7V

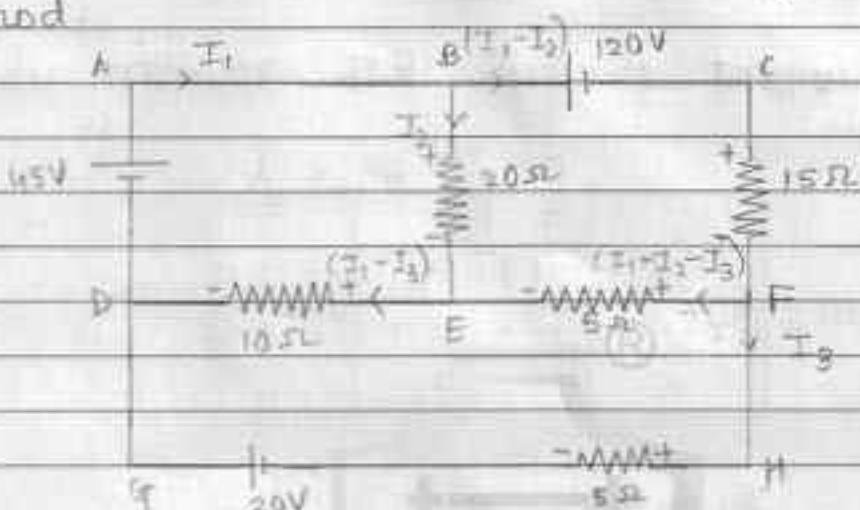Q3] Determine the current through  $20\Omega$  resistor in the circuit shown below using KVL, KCL method



Sol:

Applying KVL in loop ABEDA,

$$-20I_2 - 10(I_1 - I_2) + 45 = 0$$

$$-20I_2 - 10I_1 + 10I_3 + 45 = 0$$

$$10I_1 + 20I_2 - 10I_3 - 45 \quad \text{---(1)}$$

Applying KVL in loop BCFEB,

$$-120 - 15(I_1 - I_2) - 5(I_1 - I_2 - I_3) + 20(I_2) = 0$$

$$-120 - 15I_1 + 15I_2 - 5I_1 + 5I_2 + 5I_3 + 20I_2 = 0$$

$$20I_1 - 40I_2 - 5I_3 = -120 \quad \text{---(2)}$$

Applying KVL in loop DEFHGD,

$$10(I_1 - I_3) + 5(I_1 - I_2 - I_3) - 5I_3 + 20 = 0$$

$$10I_1 - 10I_3 + 5I_1 - 5I_2 - 5I_3 - 5I_3 + 20 = 0$$

$$15I_1 - 5I_2 - 20I_3 = -20 \quad \text{---(3)}$$

Solving eq 1, 2 & 3

$$I_1 = -0.98A, I_2 = 0.55A, I_3 = -0.378A$$

Current through  $2\Omega$  is

$$I_{20\Omega} = I_2 = \underline{2.55A}$$

Q4) Find current through  $4\Omega$  resistor using mesh analysis.



$$\text{Sol: } I_1 = 5A$$

Writing equation for supermesh

$$\therefore I_3 - I_2 = 2A$$

$$\therefore \underline{2I_3 - I_2 + I_3 = 2} \quad \text{--- (1)}$$

so Applying KVL eq<sup>n</sup> in the outerloop of supermesh.

$$-6 - 4I_3 - 2(I_2 - I_1) = 0$$

$$-6 - 4I_3 - 2I_2 + 2I_1 = 0$$

$$2I_1 - 2I_2 - 4I_3 = 6 \quad \text{--- (2)}$$

$$-2I_2 - 4I_3 = -6 \quad \text{--- (2)}$$

Applying KVL in mesh 1,

$\therefore$  On Solving eq<sup>n</sup> 1 & 2


$$\therefore I_2 = -0.67A \quad I_3 = 1.33A$$

$\therefore$  current through  $4\Omega$  is

$$I_{4\Omega} = I_3 = \underline{\underline{1.33A}}$$

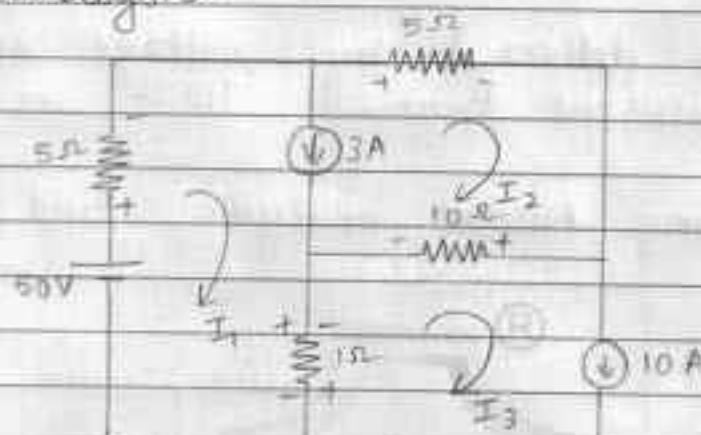Q5]

Determine the power delivered by the voltage source and the current in  $10\Omega$  resistor using mesh analysis.



Sol:

Mesh 3 contains current source.

$$\therefore \underline{I_3 = 10 \text{ A}}$$

A Writing current eq<sup>n</sup> for supermesh,

$$I_1 - I_2 = 3 \quad \text{--- (1)}$$

Applying KVL in outerloop of supermesh.

$$-5I_2 - 10(I_2 - I_3) - 1(I_1 - I_3) + 50 - 5I_1 = 0$$

$$-5I_2 - 10I_2 + 10I_3 - I_1 + I_3 + 50 - 5I_1 = 0$$

$$-6I_1 - 15I_2 + 11I_3 = -50$$

$$-6I_1 - 15I_2 + 11(10) = -50$$

$$-6I_1 - 15I_2 = -160 \quad \text{--- (2)}$$

$\therefore$  On solving eq<sup>n</sup> 1 & 2

$$\underline{I_1 = 9.76 \text{ A}} \quad \underline{I_2 = 6.76 \text{ A}}$$

$\therefore$  current through  $10\Omega$  is

$$I_{10\Omega} = I_2 - I_3 = I_3 - I_2 = 10 - 6.76 = \underline{3.24 \text{ A}}$$

Power diss. delivered by 50 V is


$$P = IV = 9.76 \times 50 = \underline{488 \text{ W}}$$

Power delivered by voltage source is 488 W  
and current through  $10\Omega$  is 3.24 A

Q] By using Nodal analysis find  $V_1$ ,  $V_2$



Sol<sup>r</sup>.

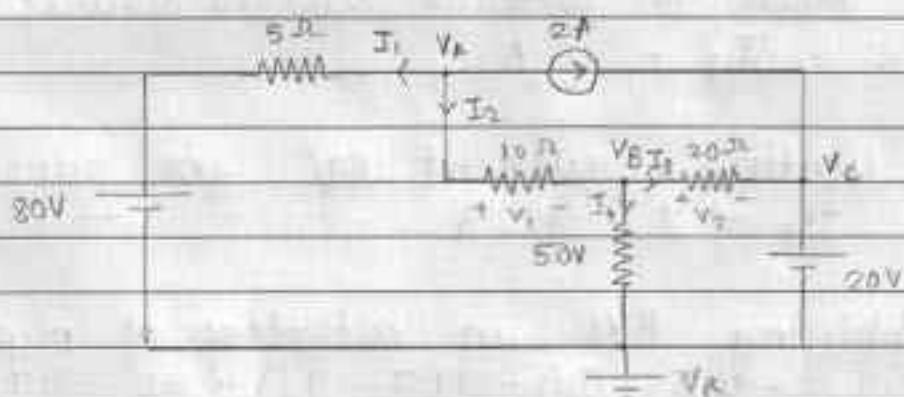

Assuming all currents are moving away from nodes.

Applying KCL at node A,

$$I_1 + I_2 + 2 = 0$$

$$\frac{V_B}{5} + \frac{V_A - V_B}{10} - 80 + \frac{V_A - V_B}{2} + 2 = 0$$

$$0.2V_A - 16 + 0.1V_A - 0.1V_B - 80 + 2 = 0$$

$$\therefore 0.3V_A - 0.1V_B = 14 \quad \text{--- (1)}$$

Applying KCL at node B,

$$\frac{V_A - V_B}{10} = \frac{V_B - V_R}{50} + \frac{V_B - V_C}{20}$$

$$0.1 V_A - 0.1 V_B = 0.02 V_B + 0.05 V_B - 0.05 V_C$$

$$\therefore 0.1 V_A - 0.17 V_B + 0.05 V_C = 0 \quad \text{---(2)}$$

Applying KCL at node C,

~~$$\frac{V_C - V_R}{20} + \frac{V_C - V_B}{50} = 0$$~~

$$V_C = 20 \text{ V} \quad \text{---(3)}$$

∴ Eq<sup>n</sup> 2 becomes

$$0.1 V_A - 0.17 V_B = -1 \quad \text{---(4)}$$

∴ On solving eq<sup>n</sup> 1 & 4

$$V_A = 60.4 \text{ V}, \quad V_B = 41.46 \text{ V}$$

$$\therefore V_1 = V_A - V_B = 18.94 \text{ V}$$

$$V_2 = V_B - V_C = 21.46 \text{ V}$$

∴  $V_1$  &  $V_2$  are 18.94 V and 21.46 V  
respectively.

## TUTORIAL 4

4.5

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 4

Page :- 1

Q1] An alternating current varying sinusoidally with 50Hz has an rms value of 20A. write down the equation for the instantaneous value and find this value 0.0025 sec. After passing through a positive maximum value. At what time measured from a positive maximum value will the instantaneous current be 14.14 A?

Sol<sup>n</sup>:

Given,

$$f = 50 \text{ Hz}$$

$$I_{\text{rms}} = 20 \text{ A}$$

$$t_1 = 0.0025 \text{ s}$$

$$I_{\text{inst.}} = 14.14 \text{ A}$$

To find,

$$t = ?$$

Solution,

$$\therefore f = 50$$

$$\therefore \omega = 2\pi f = 314.15 \text{ rad} = 100\pi$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} \quad \therefore I_0 = \underline{28.28 \text{ A}}$$

$$\therefore I = I_0 \sin(\omega t) \quad \dots \text{eq for instantaneous value}$$

$$I = 28.28 \sin(314.15 t)$$

$$\text{at } t = 0.0025 \text{ sec.}$$

$$\therefore I = 28.28 \sin(314.15 \times 0.0025)$$

$$I = 28.28 \sin(45)$$

$$\boxed{I = 20 \text{ A}}$$

Now, for positive maximum,

$$I = I_0 \cos \omega t$$

$$\frac{14.14}{28.28} = \cos 100\pi t$$

$$\therefore t = \frac{60}{100\pi} = \frac{1}{300}$$

$$\therefore t = \frac{1}{300} \text{ sec}$$

By for  
 $\therefore$  Instantaneous value is  $I = 28.28 \sin(100\pi t)$   
 Instantaneous current: 20 A

Time measured from positive maximum is  
 $1/300$  sec

Q3) Find average value and rms value of the following waveform.

a) Sol:


$$\text{Here, } V = V_m \sin \theta$$

∴ ~~average, we add~~

Average value (half period)

$$V_{avg} = \frac{1}{\pi} \int_{\pi/4}^{\pi} V_m \sin \theta d\theta$$
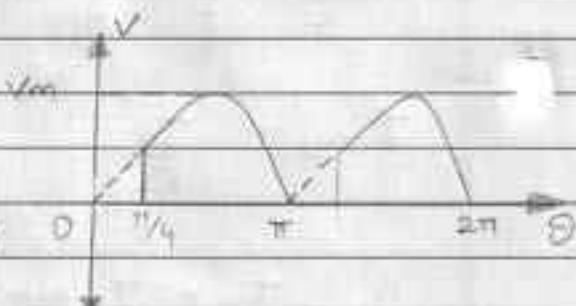
$$= -\frac{1}{\pi} [V_m \cos \theta]_{\pi/4}^{\pi}$$



$$V_{avg} = -\frac{V_m}{\pi} (-1.707)$$

$$\therefore V_{avg} = 0.543 V_m$$

RMS value,


$$\begin{aligned} \therefore V_{\text{rms}} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \theta)^2 d\theta} \\ &= \sqrt{\frac{1}{2\pi} V_m^2 \int_0^{2\pi} \sin^2 \theta d\theta} \\ &= \sqrt{\frac{V_m^2}{2\pi} \left[ \frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^{2\pi}} \\ &= V_m \sqrt{\frac{1}{2} - \frac{1}{8\pi}} \end{aligned}$$

$$V_{\text{rms}} = 0.674 V_m$$

$$\therefore V_{\text{avg}} = 0.543 V_m \quad \& \quad V_{\text{rms}} = 0.674 V_m$$

b) Here,

$$V = \frac{V_m t}{T}$$

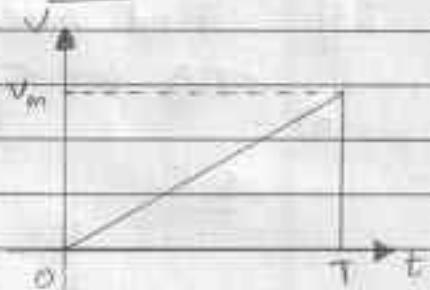

Average value,

$$\begin{aligned} V_{\text{avg}} &= \frac{1}{T} \int_0^T \frac{V_m t}{T} dt \\ &= \frac{V_m}{T^2} \int_0^T t dt \\ &= \frac{V_m}{T^2} \left[ \frac{t^2}{2} \right]_0^T \\ &= \frac{V_m \times T^2}{T^2 \times 2} = \frac{V_m}{2} \end{aligned}$$

$$V_{\text{avg}} = 0.5 V_m$$

RMS value,

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{V_m}{T} t\right)^2 dt}$$

$$\begin{aligned} &= \sqrt{\frac{V_m^2}{T^3} \left[ \frac{t^3}{3} \right]_0^T} \\ &= \frac{V_m}{\sqrt{3}} \end{aligned}$$

$$\therefore V_{\text{rms}} = 0.577 V_m$$

$$\therefore V_{\text{avg}} = 0.543 V_m \quad \& \quad V_{\text{rms}} = 0.577 V_m$$


Q3] Find average value and rms value of the following waveforms.

a)

Sol:-

$$V = V_m \sin \theta \quad \frac{\pi}{4} < \theta < \pi$$

Average value

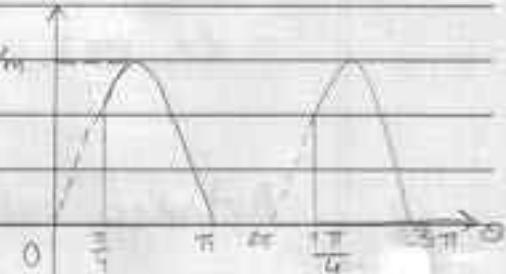

$$\begin{aligned} V_{\text{avg}} &= \frac{1}{2\pi} \int_{\pi/4}^{\pi} V_m \sin \theta d\theta \\ &= -\frac{1}{2\pi} V_m [\cos \theta]_{\pi/4}^{\pi} \\ &= -\frac{V_m}{2\pi} (-1.407) \end{aligned}$$

$$V_{\text{avg}} = 0.242 V_m$$

RMS Value,

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{-\pi/2}^{\pi} (V_m \sin \theta)^2 d\theta}$$

$$= V_m \sqrt{\frac{1}{2\pi} \int_{-\pi/2}^{\pi} 1 - \cos 2\theta \frac{d\theta}{2}}$$

$$= V_m \sqrt{\frac{1}{2\pi} \left( \frac{\theta}{2} - \frac{\sin 2\theta}{4} \right)_{-\pi/2}^{\pi}}$$

$$= V_m \sqrt{\frac{3}{16} - \frac{1}{8\pi}}$$

$$V_{rms} = 0.476 V_m$$


$$\therefore V_{avg} = 0.272 V_m, V_{rms} = 0.476 V_m$$

Sol:

$$V = \frac{V_m t}{T}$$

$$V = t \quad 0 \leq t \leq 1$$

$$= 0.5t \quad 0 \leq t \leq 2$$

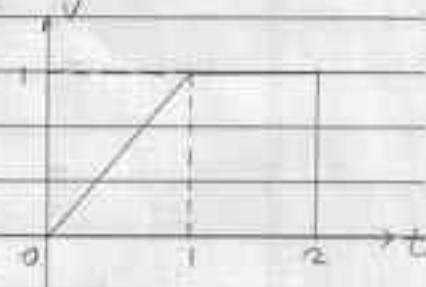

Average value,

$$V_{avg} = \frac{1}{2} \left[ \int_0^1 t dt + \int_1^2 0.5t dt \right]$$

$$= \frac{1}{2} \left[ \frac{t^2}{2} \right]_0^1 + \frac{1}{2} \left[ \frac{0.5t^2}{2} \right]_1^2$$

$$= 0.25 + 0.5$$

$$V_{avg} = 0.75 V$$

RMS value,

$$\therefore V_{rms} = \sqrt{\int_0^2 (0.5t)^2 dt}$$

$$= \sqrt{\frac{1}{4} \left[ \frac{t^3}{3} \right]_0^2}$$

$$V_{rms} = \sqrt{\frac{2}{3}} \approx 0.816 V$$

$$\therefore V_{avg} = \underline{0.75 V} \quad V_{rms} = \underline{0.816 V}$$

Q4] Find average value and rms value of the following waveforms.

a) Sol<sup>n</sup>:

$$v = V_m \sin \theta$$

Average value,

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \theta \, d\theta$$

$$= \frac{V_m}{\pi} [\cos \theta]_0^\pi$$

$$= \frac{2}{\pi} V_m$$

$$\therefore V_{avg} = \underline{0.637 V_m}$$

RMS value,

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \theta)^2 \, d\theta}$$


$$= V_m \sqrt{\frac{1}{2\pi} \int_0^{2\pi} 1 - \frac{1-\cos 2\theta}{2} \, d\theta}$$

$$= V_m \sqrt{\frac{1}{2\pi} \left[ \frac{\theta}{2} - \frac{\sin 2\theta}{\pi} \right]_0^{2\pi}}$$

$$= V_m \sqrt{\frac{1}{2}}$$

$$V_{rms} = \underline{0.707 V_m}$$
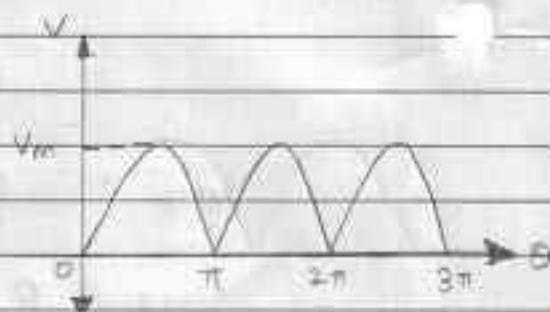
$$\therefore V_{avg} = \underline{0.637 V_m}, \quad V_{rms} = \underline{0.707 V_m}$$



b) Sol:

$$V = \frac{V_m t}{T}$$

$$V = \frac{2V_m t}{T} \quad 0 < t < \frac{T}{2}$$

$$= 0 \quad \frac{T}{2} < t < T$$



Average value,

$$V_{avg} = \frac{1}{T/2} \int_0^{T/2} \frac{2V_m t}{T} dt$$

$$= \frac{2V_m}{T/2} \left[ \frac{t^2}{2} \right]_0^{T/2}$$

$$= \frac{V_m}{2}$$

$$V_{avg} = 0.5 V_m$$

RMS value,

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^{T/2} (V_m)^2 dt}$$

$$= \sqrt{\frac{1}{T} \cdot \frac{T}{2} V_m^2} = \sqrt{\frac{1}{T} V_m^2 \left[ \frac{T}{2} \right]}$$

$$= \sqrt{\frac{V_m^2}{T} \times \frac{T}{2}}$$

$$V_{rms} = 0.707 V_m$$

$$\therefore V_{avg} = 0.5 V_m, \quad V_{rms} = 0.707 V_m$$

5] Find the resultant of following voltages

a)  $e_1 = 20 \sin \omega t, e_2 = 30 \sin (\omega t - \pi/4), e_3 = 40 \cos (\omega t + \pi/6)$

Sol<sup>n</sup>:  $e_3 = 40 \cos (\omega t + \pi/6)$   
 $= -40 \sin (\omega t + \pi/6 - \pi/2)$   
 $e_3 = -40 \sin (\omega t - \pi/3)$

$$\begin{aligned}e_r &= e_1 + e_2 + e_3 \\&= 20 \angle 0^\circ + 30 \angle -45^\circ + -40 \angle -60^\circ \\&= 25.1 \angle 32.33^\circ\end{aligned}$$

$$\therefore e = 25.1 \sin (\omega t + 32.33^\circ)$$

b)  $v_1 = 147.3 \cos (\omega t + 98.1^\circ), v_2 = 294.6 \cos (\omega t + 45^\circ),$   
 $v_3 = 88.4 \sin (\omega t + 135^\circ)$

Sol<sup>n</sup>:  $v_1 = 147.3 \sin (\omega t + 188.1^\circ)$   
 $v_2 = 294.6 \sin (\omega t + 45^\circ)$   
 $v_3 = 88.4 \sin (\omega t + 135^\circ)$

$$\begin{aligned}v_r &= v_1 + v_2 + v_3 \\&= 147.3 \angle 188.1^\circ + 294.6 \angle 45^\circ + 88.4 \angle 135^\circ \\&= 25.1 \angle 90^\circ\end{aligned}$$

$$v = 25.1 \sin (\omega t + 90^\circ)$$

c)  $e_1 = 25 \sin \omega t$ ,  $e_2 = 30 \sin (\omega t + \pi/6)$ ,  $e_3 = 30 \cos \omega t$   
 $e_4 = 20 \sin (\omega t - \pi/6)$

Sol<sup>r</sup>:

$$e_3 = 30 \cos \omega t$$

$$e_3 = -30 \sin (\omega t - 90^\circ)$$

$$e = e_1 + e_2 + e_3 + e_4$$

$$\approx 25 \angle 0 + 30 \angle 30^\circ - 30 \angle -90^\circ + 20 \angle -30^\circ$$

$$e = 46.75 \angle 27.13^\circ$$

R

$$\therefore e = 46.75 \sin (\omega t + 27.13^\circ)$$

d)  $v_1 = 60 \cos \omega t$ ,  $v_2 = 40 \sin (\omega t - \pi/3)$ ,  $v_3 = 15$

Sol<sup>r</sup>:

$$v_1 = 60 \cos \omega t$$

$$v_1 = -60 \sin (\omega t - 90^\circ)$$

(1st quadrant - 180° - Classified)

$$v = v_1 + v_2 + v_3$$

$$= -60 \angle -90^\circ + 40 \angle -60^\circ + 15 \angle 0^\circ$$

$$= 43.22 \angle 35.92^\circ$$

$$v = 43.22 \sin (\omega t + 35.92^\circ)$$

TUTORIAL 5

45

Subject:- BEE

Experiment / Tutorial / Assignment No. - 5

Page :- 1

An alternating voltage  $80 + j60 \text{ V}$  is applied to a circuit and the current flowing is  $4 - j2 \text{ A}$   
 Find a) impedance b) power consumed c) phase angle  
 d) power factor.

SOL:

Given,

$$V = 80 + j60 \text{ V} = 100 \angle 37^\circ \text{ V}$$

$$i = 4 - j2 \text{ A} = 2\sqrt{5} \angle -26.56^\circ \text{ A}$$

To find,

z, Power,  $\phi$ , Pf = ?

Formula,

$$\text{i)} z = \frac{V}{I}, \text{ ii)} P = VT \cos \phi, \text{ iii)} Pf = \cos \phi$$

Solution,

$$\text{i)} z = \frac{V}{I} = \frac{80 + j60}{4 - j2} = 22.36 \angle 63.43^\circ$$

$$\text{ii)} \text{ Real Power} = VT \cos \phi = 200 \text{ W}$$

$$\text{iii)} \text{ Phase angle } (\phi) = 63.43^\circ$$

$$\text{iv)} Pf = \cos \phi = 0.447 \text{ (lagging)}$$

$$\therefore \text{a) Impedance} = 22.36 \Omega$$

$$\text{b) Power consumed} = 200 \text{ W}$$

$$\text{c) Phase angle} = 63.43^\circ$$

$$\text{d) Power factor} = 0.447 \text{ (lagging)}$$

Q2]

An AC circuit has following voltage and current  
 $V = 325 \sin 314t$ ,  $i = 65 \sin (314t - 1.57)$ . Find (i) frequency  
(ii) RMS value of voltage and current (iii) impedance  
(iv) power factor

Soln: Given,

$$V = 325 \sin 314t$$

$$i = 65 \sin (314t - 1.57)$$

To find

if  $f$ ,  $V_{rms}$ ,  $I_{rms}$ ,  $Z$ ,  $Pf = ?$ 

Formula.

$$\text{i)} \omega = 2\pi f, \quad \text{ii)} V_{rms} = V_0/\sqrt{2}, \quad \text{iii)} I_{rms} = I_0/\sqrt{2}$$

$$\text{iv)} Z = \frac{V_0}{I_0}, \quad \text{v)} Pf = ?$$

Solution.

$$\omega = 2\pi f$$

$$f = \frac{2\pi}{\omega} = \frac{2\pi}{314} \approx 50 \text{ Hz}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{325}{\sqrt{2}} = 229.81 \text{ V}$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} = \frac{65}{\sqrt{2}} = 45.96 \text{ A}$$

$$Z = \frac{V_0}{I_0} = \frac{325}{65} = 5 \Omega$$

$$Pf = \cos \phi = \cos (1.57) = 0.99 \quad (\text{lagging})$$

- $\therefore$  a) Frequency = 50 Hz, b)  $V_{rms} = 229.81 \text{ V}$ , c)  $I_{rms} = 45.96 \text{ A}$   
d)  $Z = 5 \Omega$ , e) Power factor = 0.99 (lagging)

Q3] In a series circuit containing resistance and inductance, the current and voltage are expressed as  $i(t) = 5 \sin(314t + 2\pi/3)$  and  $V(t) = 20 \sin(314t + \frac{\pi}{6})$   
 a) what is the impedance of the circuit? b) what are the values of resistance, inductance and power factor c) what is the average power drawn by circuit?

Sol:

Given,

$$V = 20 \sin(314t + \frac{\pi}{6}) = 20 \angle 150^\circ \text{ V}$$

$$I = 5 \sin(314t + 2\pi/3) = 5 \angle 120^\circ \text{ A}$$

To find,

i)  $Z$ , R, L, Pf, Pavg.

Formula,

$$\text{i) } Z = \frac{V}{I}, \text{ ii) } X_L = \omega L, \text{ iii) } Pf = \cos \phi,$$

$$\text{iv) } P = VI \cos \phi$$

Solution,

$$Z = \frac{V}{I} = \frac{20 \angle 150^\circ}{5 \angle 120^\circ} = 4 \angle 30^\circ \Omega,$$

$$\therefore Z = 3.46 + j2$$

$$\therefore R = 3.46 \Omega,$$

$$\text{ii) } X_L = \omega L$$

$$L = \frac{X_L}{\omega} = \frac{2}{314} = 0.0063 \text{ H,}$$

$$Pf = \cos \phi = \cos(30^\circ) = 0.866 \quad (\text{lagging})$$

$$P = VI \cos \phi = 43.3 \text{ W,}$$

- i) Impedance =  $4\ \Omega$ ,
- ii) Resistance =  $3.46\ \Omega$ ,
- iii) Inductance =  $0.0063\ H$ ,
- iv) Power factor =  $0.866$  (lagging)
- v) Power drawn =  $43.3\ W$ ,

Q4] The voltage applied to a circuit is  $e = 100 \sin(\omega t + 30^\circ)$  and current flowing in the circuit is  $i = 15 \sin(\omega t + 60^\circ)$ . Determine impedance, resistance, reactance, power and power factor.

Sol:

Given,

$$e = 100 \sin(\omega t + 30^\circ) = 100 \angle 30^\circ$$

$$i = 15 \sin(\omega t + 60^\circ) = 15 \angle 60^\circ$$

To find,

- i) Impedance ( $=$ ), ii)  $R$ , iii)  $X_L$ , iv)  $P$  &  $P_f$ .

Formula,

$$\text{i)} Z = \frac{V}{I} \quad \text{ii)} P = VI \cos \phi \quad \text{iii)} P_f = VI \cos \phi$$

Solution,

$$Z = \frac{V}{I} = 6.67 \angle -30^\circ \Omega$$

$$Z = 5.77 - 3.33 j$$

$$\therefore R = 5.77 \Omega$$

$$X_L = 3.33 \Omega$$

$$P = VI \cos \phi = 649.5 \text{ W}$$

$$P_f = \cos \phi = \cos(30) = 0.866 \text{ (reading)}$$

i) Impedance =  $6.67 \Omega$

ii) Resistor =  $5.77 \Omega$       iii) reactance =  $3.33 \Omega$

w) Power = 649.5 W v) Power factor = 0.866 (leading)

Q5] A load consisting of a capacitor in series with a resistor has an impedance of  $50\ \Omega$  and pf. 0.707 leading. The load is connected in series with  $40\ \Omega$  resistor across AC supply and resulting current is 3A. Determine the supply voltage and overall phase angle sol:

Given:

$$Z = 50\ \Omega$$

$$\text{pf} = 0.707 \text{ (leading)}$$

$$R = 40\ \Omega$$

$$I = 3\text{A}$$

To find,

V, phase angle?

Formula,

$$\text{i)} \text{pf} = \cos \phi \quad \text{ii)} V = IR$$

Solution,

$$\text{pf} = \cos \phi \Rightarrow \phi = 45^\circ$$

$$\therefore Z = 50 \angle -45^\circ$$

$$= 35.35 - 35.35j$$

$$Z = 75.35 - 35.35j$$

$$Z = 83.23 \angle -25.13^\circ$$

$$V = IZ = 3 \times 83.23 = 249.69\text{V}$$

$$\phi = -25.13^\circ$$

$\therefore$  Voltage =  $249.69\text{V}$  & phase angle =  $-25.13^\circ$

Q6] A leaky capacitor  $Z_c = 74.5 \Omega$  is in series with a coil  $Z_L = 40 \Omega$  & a resistor  $R = 56 \Omega$ . When voltage  $V = 200V$  is applied,  $I = 2.5A$  & the p.d across  $R$  &  $Z_L$  combined is 194V. Find the loss in the capacitor.

Sol:

Given,

$$Z_c = 74.5 \Omega, Z_L = 40 \Omega \\ R = 56 \Omega, V = 200V$$

To find,

Power loss?

Formula

$$P = I^2 R$$

solution,

$$Z_{\text{Total}} = \frac{194}{2.5} = 77.6 \Omega$$

$$\sqrt{(R+r_1)^2 + X_L^2} = 77.6 \\ (56+r_1)^2 + X_L^2 = 77.6^2 \quad \text{--- (1)}$$

or

$$\text{Also } \sqrt{r_1^2 + X_L^2} = 40 \\ r_1^2 + X_L^2 = 40^2 \quad \text{--- (2)}$$

on solving 1 & 2

$$r_1 = 11.48 \Omega \quad X_L = 38.32 \Omega$$

$$\sqrt{r_1^2 + X_C^2} = 74.5 \quad \text{--- (3)}$$

$$Z_T = \frac{200}{2.5} = 80$$

$$\sqrt{(R+r_2+x_c)^2 + (X_L-X_C)^2} = 80$$

$$\sqrt{(56+11.48+r_2)^2 + (38.32-x_c)^2} = 80$$

$$(56+11.48+r_2)^2 + (38.32-x_c)^2 = 80^2$$

$$4553.55 + 134.96r_2 + r_2^2 + 1468.42 - 75.64x_c + x_c^2 = 80^2$$

∴ Now eq<sup>n</sup> 3 becomes,

$$134.96r_2 - 75.64x_c = -5172.22$$

$$x_c = 1.76r_2 + 67.49 \quad \text{---}$$

$$\therefore r_2^2 = 5550.25 - x_c^2$$

$$= 5550.25 - (1.76r_2 + 67.49)^2$$

$$r_2 = 3.92$$

∴ Power consumed loss in capacitor

$$P = I^2 R r_L = (2.5)^2 \times (3.92) = 24.5 \text{ W},$$

∴ Power loss in capacitor is  $\approx 4.5 \text{ W}$ ,

## TUTORIAL 6

45

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 6

Page - 1

RLC

- Q1] A RLC series circuit has a current which lags the applied voltage by  $45^\circ$ . The voltage across the inductance has maximum value equal to twice the maximum value of voltage across the capacitor. Voltage across the inductance is  $300\sin(1000t)$  and  $R = 20\Omega$ . Find the value of inductance and capacitance.

Sol:

Given,

$$\phi = 45^\circ$$

$$V = 300 \sin(1000t)$$

$$R = 20\Omega, V_L = 2V_C$$

To find,

$$L, C \Rightarrow$$

Formula,

$$X_L = 2\pi f L = 63.6\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{63.6} \Omega$$

solution,

$$V_L = 2V_C$$

$$2X_L = 2X_C$$

$$X_L = 2X_C$$

$$\cos \phi = \frac{R}{Z} \Rightarrow Z = \frac{20}{\cos 45^\circ} = 28.28\Omega$$

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$28.28^2 = 20^2 + (X_C)^2$$

$$\therefore X_C = 20\Omega$$


$$\therefore X_C = \frac{1}{2\pi f C} \Rightarrow C = 50\mu F$$

$$X_L = 2X_C \rightarrow 40\Omega$$

$$\begin{aligned} X_L &= \omega L \\ L &= 0.04 \text{ H} \end{aligned}$$

Inductance = 0.04 H & capacitance = 50 μF

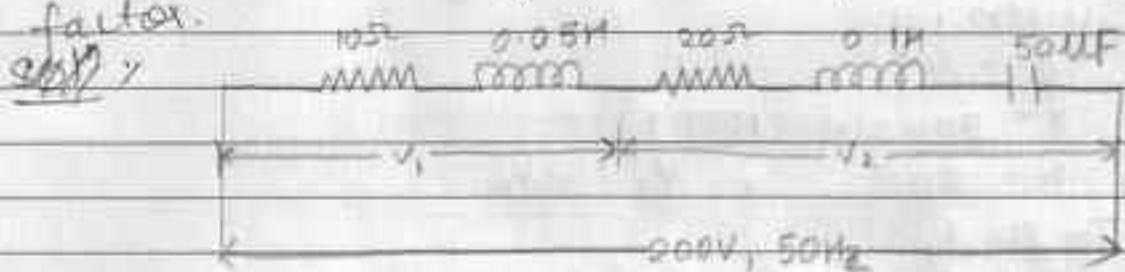- Q3) Draw a vector diagram for circuit shown  
Find the value of current,  $V_1$  &  $V_2$  & power factor.



Sol:

Given,

$$L_1 = 0.05 \text{ H}, R_2 = 20\Omega$$

$$L_2 = 0.1 \text{ H}, C = 50 \mu\text{F}$$

$$R_1 = 10\Omega$$

To find,

$$I, V_1, V_2, \text{ Pf} = ?$$

Formula,

$$\text{i) } \frac{I}{R} = \frac{V}{R} = \text{ii) } \text{Pf} = \cos \phi$$

Solution

$$X_{L_1} = 2\pi f L_1 = 15.7 \Omega$$

$$X_{L_2} = 2\pi f L_2 = 31.4 \Omega$$

$$X_C = \frac{1}{2\pi f C} = 63.67 \Omega$$

$$Z = 30 - 16.57j \Rightarrow 34.27 \angle -28.9^\circ \Omega$$

$$\therefore I = \frac{200 \angle 0}{34.27 \angle -28.9} = 5.83 \angle 28.9 A$$

$$Z_1 = R_1 + jX_{L1} = 10 + 1.57j \Omega = 18.6 \angle 57.3^\circ \Omega$$

$$Z_2 = R_2 + j(X_L - X_C) = 20 + j(31.4 - 63.67)$$

$$= 37.93 \angle -58.21^\circ \Omega$$

$$Z_T = (R_1 + R_2) + j(X_L + X_1 - X_C) = 30 + j(-16.57)$$

$$\bar{Z}_T = 34.27 \angle -28.9^\circ \Omega$$

$$\bar{V}_1 = I \bar{Z}_1 = 5.83 \angle 28.9^\circ \times 18.6 \angle 57.3^\circ$$

$$V_1 = 108.56 \angle 85.3^\circ V$$

$$\bar{V}_2 = I \bar{Z}_2 = 5.83 \angle 28.9^\circ \times 34.27 \angle -28.9^\circ$$

$$= 220.34 \angle -29.31^\circ V$$

$$\cos \phi = \cos \phi = 0.875$$


$$I = 5.83 A$$

$$V_1 = 108.56 V$$

$$V_2 = 220.34 V$$

$$P_f = 0.875$$

Phasor diagram:

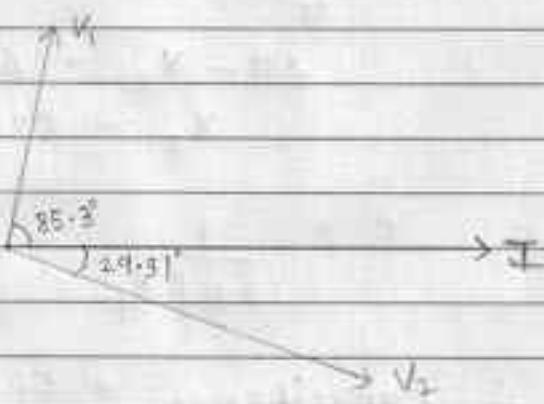

Q3] A coil of resistance  $3\Omega$  and inductance  $0.22\text{H}$  is connected in series with imperfect capacitor. When such a series circuit is connected across a supply of  $200\text{V}$ ,  $50\text{Hz}$ , it has been observed that their combined impedance is  $(3.8 + j6.4)\Omega$ . Calculate the capacitance and its equivalent capacitor's resistance.

Sol:

Given,  
 $R = 3\Omega$ ,  $L = 0.22\text{H}$ ,  $V = 200\text{V}$ ,  $f = 50\text{Hz}$ ,

$$Z = (3.8 + j6.4)\Omega$$

To find,

$$C = ? \quad X_C = ?$$

Formula,

$$C = \frac{1}{2\pi f X_C}$$

Solution

$$X_L = 2\pi f L = 69\Omega$$

$$\therefore Z = 3.8 + j6.4 \quad \text{--- (1)}$$

$$Z = (R + jX_C) + j(69 - X_C) \quad \text{--- (2)}$$

∴

$$\therefore 69 - X_C = 6.4 \quad \therefore 3.8 = 3 + R$$

$$\therefore X_C = 62.6\Omega \quad R = 0.8\Omega$$

$$C = \frac{1}{2\pi f X_C} = 50.87 \mu\text{F}$$

$$\therefore \text{Capacitance} = 50.87 \mu\text{F}, \text{ Resistance} = 0.8\Omega$$

## Resonance

Q1)

A voltage  $V(t) = 10 \sin \omega t$  is applied to a series RLC circuit. At resonant frequency voltage across capacitor is found to be 500V. The bandwidth of the circuit is known to 400 rad/sec and impedance at resonance is 10Ω. Determine resonant frequency, upper & lower cut off frequencies, L & C.

Soln:

Given,

$$BW = 400 \text{ rad/s}$$

$$V_m = 500 \text{ V}, V = 10 \sin \omega t$$

$$R = 1 \Omega$$

To find,

$$f_r, f_1, f_2, L \& C = ?$$

Formula,

$$\text{i) Bandwidth} = \frac{R}{L}, \text{ ii) } f_r = \frac{1}{2\pi\sqrt{LC}}, \text{ iii) Lower: } f_L = f_r - \frac{R}{4\pi L}$$

$$\text{iv) Upper: } f_U = f_r + \frac{R}{4\pi L}$$

Solution,

$$V = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 \text{ V}$$

$$BW = \frac{R}{L} = \frac{1}{400}$$

$$L = 0.0025 \text{ H}$$

$$Q = \frac{V_C}{V} = \frac{500}{7.07} = 70.72,$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow C = 0.5 \mu F$$

$$\text{Resonant frequency } f_r = \frac{1}{2\pi\sqrt{LC}} = 4503.86 \text{ Hz}$$

$$(\text{lower cut frequency } f_l) f_l = R = 4475 \text{ Hz}$$

$$(\text{upper cut frequency } f_u) f_u = R = 4538 \text{ Hz}$$

$$\therefore \text{Resonant frequency} = 4503.86 \text{ Hz}$$

$$\text{Lower cut frequency} = 4475 \text{ Hz}$$

$$\text{Upper cut frequency} = 4538 \text{ Hz}$$

$$\text{Inductance} = 0.0025 \text{ H}$$

$$\text{capacitance} = 0.5 \mu\text{F}$$

Q1) Impedance of a circuit is observed to be decreasing from 1Hz to 100Hz beyond 100Hz, impedance start increasing. Find the value of circuit elements if the power drawn by the circuit is 100W at 100Hz, when the current is 1A. Power factor of the circuit at 40Hz is 0.707.

Sol:

Given,

$$f_0 = 100 \text{ Hz}, P = 100 \text{ W}$$

$$\text{where } I = 1 \text{ A}, f_1 = 1 \text{ Hz}$$

To find

$$R, L, C = ?$$

Series formula,

$$\text{i)} P = I^2 R, \text{ ii)} f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Solution,

$$\text{Lower cut off frequency } (f_1) = f_c = \frac{R}{4\pi L}$$

$$1 = 100 = \frac{R}{4\pi L}$$

$$\frac{R}{4\pi L} = 99$$

$$\frac{R}{L} = 396\pi \quad \text{--- (1)}$$

$\therefore P = 100W$  at when  $I = 1A$

$$P = I^2 R$$

$$100 = (1)^2 R$$

$$\therefore R = 100 \Omega$$

From (1)

$$\frac{100}{L} = 396\pi$$

$$L = 0.08 \text{ H}$$

$$\text{At resonance, } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore C = 31.66 \mu\text{F}$$

∴ Resistor =  $100\Omega$

Inductance =  $0.08 \text{ H}$

Capacitance =  $31.66 \mu\text{F}$

Q3)

An inductance coil having a resistance of  $2\Omega$  and an inductance of  $200\text{ mH}$  is connected in parallel with a variable capacitor. This parallel combination is connected in series with a resistance of  $8000\text{ }\Omega$ . A voltage of  $280\text{ V}$  at frequency of  $10^6\text{ Hz}$  is applied across the circuit. Calculate i) capacitance at resonance ii) Q factor of the circuit iii) dynamic impedance of circuit iv) total circuit current.

sol:


Given,

$$R_p = 8000\text{ }\Omega$$

$$R = 2\Omega$$

$$L = 0.2\text{ H}$$

$$V = 280\text{ V} \quad f_r = 10^6$$

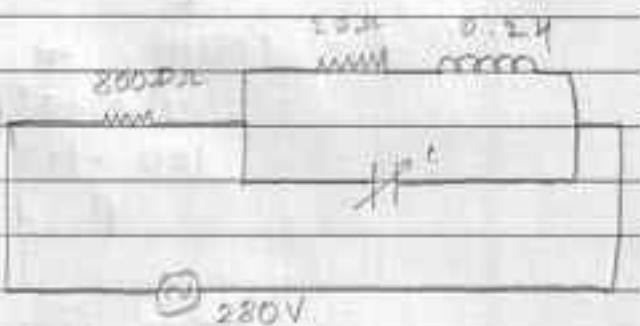

To find,

$C_r, Q, Z_d, I_T \dots ?$

Formula,

$$\text{i)} f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{ii)} Q = \frac{2\pi f_r L}{R} \quad \text{iii)} Z_d = \frac{L}{CR}$$

(a)

Solution.

$$f_r = \frac{1}{2\pi\sqrt{LC}} \Rightarrow \frac{1}{C} = 2\pi f_r \sqrt{L}$$

$$\therefore C = 1.269 \times 10^{-13}\text{ F},$$

$$Q = \frac{2\pi f_r L}{R} = 62800$$

$$Z_d = \frac{L}{CR} = 7.88 \times 10^{10}\text{ }\Omega$$

$$Z_1 = Z_1 + Z_2 = 7.883 \times 10^{10} \Omega$$

$$I = \frac{230}{7.883 \times 10^{10}} = 2.99 \times 10^{-9} A$$

$$\text{Capacitance} = 1.269 \times 10^{-15} F$$

$$Q \text{ factor} = 62800$$

$$\text{Dynamic Impedance} = 7.88 \times 10^{10} \Omega$$

$$\text{Total circuit current} = 2.99 \times 10^{-9} A$$

TUTORIAL 7

Subject :- BEE

Experiment / Tutorial / Assignment No. :- 7

Page :- 1

- Q1] A 30 kVA, 24500/120V, 50 Hz transformer has a high - voltage winding resistance of 0.1 ohm and leakage resistance of 0.22 ohm. The low voltage winding resistance is 0.035 ohm and the leakage reactance is 0.012 ohm, calculate for transformer:
- Equivalent resistance as referred to both primary and secondary side.
  - Equivalent reactance as referred to both primary and secondary side.
  - Equivalent impedance as referred to both primary and secondary side.
  - copper loss at full load.

Soln:

a) Primary resistance =  $R_1$   
 Secondary resistance =  $R_2$

$$\therefore K = \frac{120}{24500} = 4.9 \times 10^{-3}$$

$$\therefore R_{eq} = R_1 + \frac{R_2}{K^2} = 0.1 + \frac{0.035}{2.4 \times 10^{-5}} = 1458.44 \Omega$$

$$R_{eq} = \underline{1458.44 \Omega}$$

$$R_{eq} = R_1 + R_2 (K^2) + 35 m\Omega$$

b) Primary reactance =  $X_{eq}$

Secondary reactance =  $X_{eq}$

$$X_{eq} = X_1 + \frac{X_2}{K^2} = 500.22 \Omega$$

$$X_{eq} = X_2 + X_1 (K^2) = 12 m\Omega$$

c) Primary impedance =  $Z_{p1}$

Secondary impedance =  $Z_{p2}$

$$\therefore Z_{p1} = \sqrt{R_{p1}^2 + X_{p1}^2}$$

$$Z_{p1} = 1541.8 \Omega$$

$$\therefore Z_{p2} = \sqrt{R_{p2}^2 + X_{p2}^2}$$

$$Z_{p2} = 0.037 \Omega$$

d) ~~Q2~~  $I_{p1} = \frac{3.0 \times 1000}{2400} = 1.22 A$

$$\text{Copper loss} = I_{p1}^2 R_{p1} = 2130.44 W$$

$$\therefore a) R_{p1} = 1458.44 \Omega$$

$$R_{p2} = 35 m\Omega$$

$$b) X_{p1} = 500.22 \Omega$$

$$X_{p2} = 12 m\Omega$$

$$c) Z_{p1} = 1541.8 \Omega$$

$$Z_{p2} = 0.037 \Omega$$

$$d) \text{Copper loss} = 2130.44 W$$

Q2] A 5 KVA, 1000/200V, 50 Hz, single phase transformer gives the following test results

No. of Load Test/O.C. Test (HV side)	1000V	0.24A	90W
S.C. Test (L.V. side)	50V	5A.	110W

calculate:

- a) The equivalent circuit constants refer to low voltage side and draw equivalent circuit diagram.

Sol:

1] for o.c. Test

$$\cos \phi = \frac{V_o}{I_o} = \frac{90}{0.24 \times 1000} = 0.375$$

$$\therefore \phi = 68^\circ$$

$$I_{10} = I_o \cos \phi = 0.09 \text{ A}$$

$$I_{20} = I_o \sin \phi = 0.27 \text{ A}$$

$$R_s = V_i = \frac{11.11 \text{ K}\Omega}{I_{10}}$$

$$X_s = \frac{V_i}{I_{20}} = \frac{1000}{0.27} = 4545.45 \Omega$$

2] for s.c. Test

$$Z_{02} = \frac{V_{sc}}{I_{sc}} = 1052 \Omega$$

$$R_{02} = \frac{V_{sc}}{I_{sc}} = \frac{110}{B^2} = 4.4 \Omega$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2}$$

$$X_{02} = 8.98 \Omega$$

∴ So the equivalent circuit referred to L.V. side can now be drawn showing all the parameter values as Turn ratio,  $K = \frac{200}{1000} = 0.2$ ,

$$\therefore R_{01} = R_{02}/K^2 = 110 \Omega$$


$$B_{02} = B$$

$$X_{01} = X_{02}/K^2 = 8.98/0.2^2$$

$$X_{01} = 224.5 \Omega$$

3] Equivalent circuit diagram
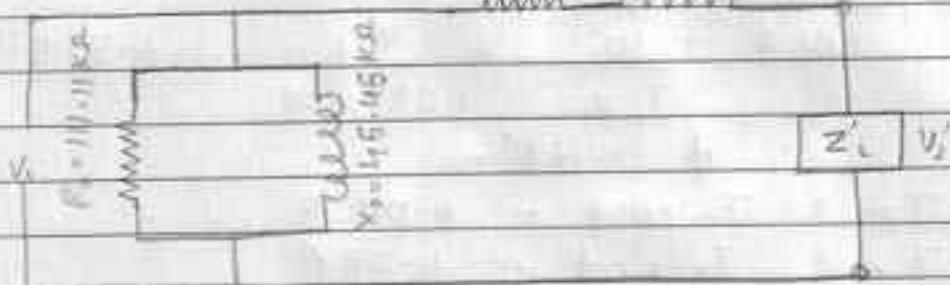
$$R_{eq} = 10 \Omega \quad X_{eq} = 224.5 \Omega$$



Q3] A 5kVA, 200/400 V, 50Hz, single-phase transformer gives the following test results:

O.C Test (L.V. side)	200 V	0.7 A	60 W
S.C. Test (H.V. side)	22 V	16 A	120 W

calculate :

- The equivalent circuit constants refer to primary side and draw equivalent circuit diagram
- Find efficiency and regulation at 0.9 pf (lead) if operating at rated load.
- Find current at which efficiency is maximum

Sol: a) i) for OC test

$$K = \frac{400}{200} = 2$$

$$\cos \phi = \frac{w_i}{V_1 I_o} = \frac{60}{0.7 \times 200} = 0.428$$

$$\therefore \phi = 64.62^\circ$$

$$\therefore T_w = T_o \cos \phi \quad , \quad I_M = I_o \sin \phi$$

$$T_o = 0.3 \text{ A}$$

$$T_M = 0.632 \text{ A}$$

$$\therefore R_s + \frac{V_1}{T_w} = 666.67 \Omega$$

$$X_s = V_1 = 316.45 \Omega$$


i) For S.C. test

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{22}{16} = 1.375 \Omega, R_{02} = \frac{W_{SC}}{I_{SC}^2} = \frac{0.47 \Omega}{16}$$

$$\therefore X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{1.375^2 - 0.47^2} = 1.29 \Omega$$

$$B_1 = \frac{R_{02}}{k^2} = \frac{0.47}{16} = 0.117 \Omega, X_01 = \frac{X_{02}}{k^2} = \frac{0.322 \Omega}{16}$$

iii) The equivalent circuit is

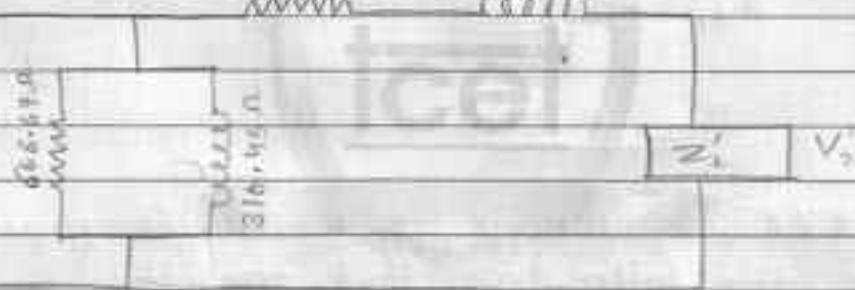

$$b) W_i = 60 \text{ W}$$

$$\therefore I_{02} = \frac{3000}{400} = 12.5 \text{ A}$$

$$\therefore W_{cu} = I_{02}^2 R_{02} = 12.5^2 \times 0.47 \\ W_{cu} = 73.43 \text{ W}$$

$$\eta = 1, \rho_f = 0.9$$

$$\eta = \frac{\rho_f \eta \times \rho_f}{\rho_f + \rho_f \times \eta + W_i + X^2 W_{cu}} = \frac{1 \times 5000 \times 0.9}{0.9 + 5000 \times 1 \times 60 + 1^2 (73.43)}$$

$$\eta = 0.9712 \times 100$$

$$\eta = 97.12 \%$$

$\therefore$  Regulation at rated load and 0.9 pf.  
 $\cos\phi = 0.9 \Rightarrow \sin\phi = 0.43$

$$\therefore \text{regulation} = \frac{I_o (R_{o2} \cos\phi + X_{o2} \sin\phi)}{V_2} \times 100$$

regulation = -0.41%.

c) current at which efficiency is maximum

$$W_i = I_{o2}^2 R_{o2}$$

$$I_{o2} = \sqrt{\frac{60}{0.42}}$$

$$I_{o2} = 12 \text{ A}$$

Q4] A 5 kVA, 250/500 V, 50 Hz, single-phase transformer gives the following test results.

No Load test / O.C Test (L.V. side)	250V	0.75A	60W
C.R. Test (H.V.) side	9V	6A	21.6W

calculate:

- The equivalent circuit constants refer to primary side and draw equivalent circuit diagram
- Efficiency at 60% of full load unity pf
- Maximum efficiency and the load at which it occurs.
- The secondary terminal voltage on full load at pf of 0.8 lagging, unity and 0.8 leading

Sol<sup>n</sup>:

a) i) for D.C Test

$$\therefore \cos\phi = \frac{w_i}{T_o V_r} = \frac{60}{250 \times 0.75} = 0.32$$

$$\phi = 71.33^\circ$$

$$\therefore I_{m0} = T_o \cos\phi = 0.75 \cos(71.33)$$

$$I_{m0} = 0.24 \text{ A}$$

$$\therefore I_m = T_o \sin\phi = 0.75 \sin(71.33)$$

$$I_m = 0.71 \text{ A}$$

$$\therefore R_o + \frac{V_r}{I_{m0}} = 1041.67 \Omega$$

$$X_{m0} + \frac{V_r}{I_m} = 352.11 \Omega$$

ii) for S.C. Test

$$\therefore K = \frac{500}{250} = 2$$

$$\therefore Z_{o2} = \frac{V_{SC}}{I_{SC}} = \frac{9}{6} = 1.5 \Omega$$

$$R_{o2} = \frac{w_{SC}}{I_{SC}^2} = \frac{21.6}{6^2} = 0.6 \Omega$$

$$\therefore X_{o2} = \sqrt{Z_{o2}^2 - R_{o2}^2} = 1.374 \Omega$$


$$R_{o1} = \frac{R_{o2}}{K^2} = \frac{0.6}{2^2}$$

$$X_{o1} = \frac{X_{o2}}{K^2} = \frac{1.374}{2^2}$$

$$R_{o1} = 0.15 \Omega$$

$$X_{o1} = 0.3435 \Omega$$

a) The equivalent circuit is

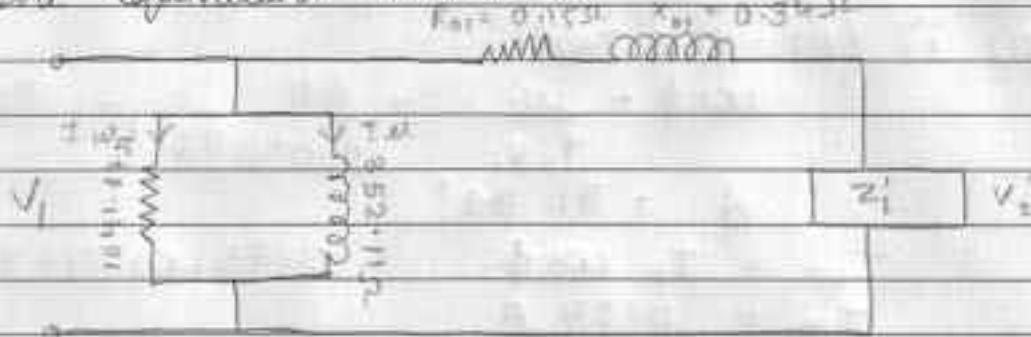

b) ~~Given~~  $W_i = 60 \text{ W}$

$$\therefore I_{o2} = \frac{5000}{500} = 10 \text{ A}$$

$$W_{cu} = I_{o2}^2 R_{o2} = 60 \text{ W}$$

$$\alpha = 0.6, \quad P_f = 1$$

$$\eta = \frac{\cos \phi \times \alpha \times W_i + \alpha \times W_{cu}}{\cos \phi \times 5 \times \alpha + W_i + \alpha \times W_{cu}} = \frac{0.6 \times 5000 \times 1}{1 \times 5000 + 0.6 + 60 + (0.6)^2 60}$$

$$\eta = 0.9735 \times 100$$

$$\therefore \eta = 97.35 \%$$

$$c) \Rightarrow KVA_{(max)} = KVA_{FL} \sqrt{\frac{W_i}{W_{cu}}} = 5000 \times \sqrt{\frac{60}{60}} = 5000 \text{ VA}$$

For maximum efficiency

$$W_i = W_{cu} = 60 \text{ W}, \quad P_f = 1$$

$$\eta = \frac{\text{load kVA} \times P_f \times 100}{\text{load kVA} \times P_f + W_i + W_{cu}} = \frac{5000 \times 1 \times 100}{5000 \times 1 + 60 + 60}$$

$$\eta = 97.65 \%$$

$$d) \because \text{regulation} = \frac{E_2 - V_2}{V_2}$$

$$\therefore I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi \rightarrow \frac{E_2 - V_2}{V_2}$$

$$\therefore E_2 - V_2 = I_2 (R_{02} \cos \phi \pm X_{02} \sin \phi)$$

$$V_2 = E_2 - I_2 (R_{02} \cos \phi + X_{02} \sin \phi)$$

For  $P_f = 0.8$  lagging

$$\cos \phi = 0.8$$

$$\sin \phi = 0.6$$

$$\therefore E_2 = 500 \text{ V}$$

$$V_2 = 500 - 10 (0.6(0.8) + 1.37(0.6))$$

$$\therefore V_2 = \underline{486.98 \text{ V}}$$

For  $P_f = 0.8$  leading

$$V_2 = 500 - 10 (0.6(0.8) - 1.37(0.6))$$

$$\therefore V_2 = \underline{503.42 \text{ V}}$$

For unity  $P_f$

$$V_2 = 500 - 10 (0.6(1)) + 0$$

$$V_2 = \underline{494 \text{ V}}$$

## REPORT ON BULLET TRAIN

On the 5th of April 2021, the Innovative Exam of BEE was conducted where everyone was supposed to give a presentation on the topic assigned by the teachers in a group of four. Group no. 12 got the topic **BULLET TRAINS**. This group consisted of roll no. 45, 46, 47 and 48 namely Ishika Sharma, Sarvesh Sharma, Aditi Shetty and Aditya Shukla respectively.

The presentation was started by Ishika Sharma (roll no. 45). She gave the introduction to the topic and her above-mentioned group members along with the points that will be covered in the presentation. She told about bullet trains in short and the brief was covered by rest of the members. Bullet trains are named so because of their appearance and speeds. Many countries have also introduced Bullet trains which will also include India soon.

Ishika also told about the history of bullet trains, Hideo Shima was the one who invented bullet trains, the first bullet train was '**Tōkaidō Shinkansen**' from 1st October 1964 also the booming sound that train made while moving through a tunnel was then corrected by taking inspiration from the bird **KINGFISHER** and many more. Ishika then handed the presentation to Sarvesh Sharma (roll no. 46) to continue the presentation.

Sarvesh started his presentation with Existing High-Speed Rail Systems by Different Countries, with the help of tables he showed Countries of different regions like Asia, Europe, Africa, United States and Australia with their top speed of Bullet Trains.

In the Asia region, China was at the topmost position with speed of 320km/hr followed by Japan, South Korea, Turkey and many more with a speed of 320, 305, 300 km/hr respectively. In the Europe region, France is at the top with a speed of 320km /hr followed by Spain, Germany, the UK, Italy with speeds of 310, 300, 300, 300 km/hr respectively. In Africa, US, Australia region, Morocco, USA & Oceania got trains with a top speed of 320, 240, 200 km/hr respectively.

Then he explained the Advantages and Disadvantages of Bullet Train whereas in the Advantages he included some of the major points like Speed, Comfort, Safety, No Overcrowding, Toughness and Bullet Trains are Eco-Friendly. In Disadvantages, he covered some important points like Cost of Construction, High Fares, Time Consuming Project, Land Acquisition and Other Issues as well. He Covered all the positive and negative points wisely. Sarvesh then requested Aditi Shetty (roll no. 47) to continue the presentation.

Bullet Trains seems to be one of the most magnificent creations of the human era. There is no comparison to this mode of transport. But, still just to make the critics clear about the significance of this transport, Aditi Shetty Roll no.47 elaborated how bullet trains are better than any other transport mode. Some of the many factors in which bullet trains are reliable are speed, safety, energy efficiency and market shares as well. Also, Aditi Shetty further explained the deadly accidents in which unfortunately many people lost their lives. A few of them were Eschede, Wenzhou, Ankara and Lodi derailment in Italy. Unfortunately, It caused an ample amount of loss to mankind and financially to the government as well. But as of now, safety measures have been increased and they are much more reliable than before. From here Aditya Shukla (roll no. 48) continued the presentation.

Aditya started by saying that Prime minister Narendra Modi proposed the first bullet train in India for the Ahmedabad-Mumbai link covering 534 km at about 300km/h speed. Aditya highlighted bullet train in India there is many bullet train project in India but the one which would be completed early is Mumbai to Ahmedabad. Japan gave Rs.79000

Crores to India. India will have to pay back till 2050 with a nominal interest of 0.1 percent. then it was followed by the ridership of bullet train Japan's Shinkansen network had the highest annual passenger ridership of any high-speed rail network until 2011, when the Chinese high-speed railway network surpassed it at 370 million passengers annually, reaching over 2.3 billion passengers in 2019. Intercity effects of the bullet train are with high-speed rail there has been an increase in accessibility within cities. It allows for urban regeneration, accessibility in cities near and far, and efficient inter-city relationships lead to high-level services to companies, advanced technology, and marketing. He concluded by saying that Bullet Train is a very good option to replace normal train as it is more efficient and does not make pollution.

Some of the most interesting actuality was shared by Aditi Shetty

So, at the end Sarvesh Ended the Presentation by saying that Bullet Trains are one of the best Magnificent Man-Made Creation.

- ISHIKA SHARMA-45
- SARVESH SHARMA-46
  - ADITI SHETTY-47
  - ADITYA SHUKLA-48